

POWER ELECTRONICS
B.E., VII Semester, Electronics & Communication Engineering
Course Code 17EC73 CIE Marks 40

RNS INSTITUTE OF TECHNOLOGY
DEPARTMENT OF ELECTRONICS AND COMMUNICATION
POWER ELECTRONICS NOTES:

MODULE-2

~~8/10/21~~

P-1
1/1

MODULE - 2

THYRISTORS

SYLLABUS

TEXT-2

MD Singh.

INTRODUCTION : ~~2.1~~ 2.1

Principle of operation 2.2

Static Anode-Cathode Characteristic : 2.3

Two Transistor Model - 2.4

Gate characteristics : 2.6

Turn ON methods 2.7

Turn OFF mechanism 2.9

Turn off methods Natural & Forced Commutation
Class A and Class-B Types - 2.10

Gate Trigger Circuit :

Resistance firing circuit, Resistance Capacitance
firing circuit UJT firing circuit

3.5 and 3.6.

INTRODUCTION

SCR → Silicon Controlled Rectifier.

Or Thyristor derived from Thyatron
and Transistor words.


Features :

1. A four layer device (PNPN)
2. A latching type of device. (on conduction jump from low cur to high current and continuous to be ON when anode cur > latching current)
3. It Can handle large power. (Voltage and cur in ~~KVA~~ range)
4. Current Controlled device with gate control for switching on.
5. It Can act as Switch with on & off state.
6. on State Voltage across device is very small ($< 1V$)
7. It Can be visualized as two transistors connected back to back.

SYMBOL


Anode

Gate.
Cathode

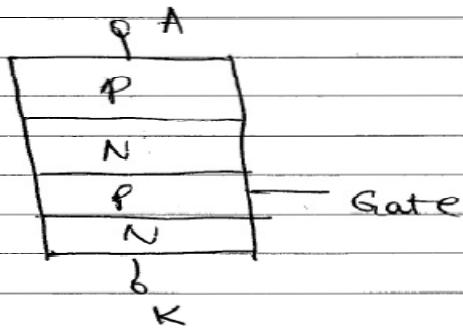

Operations :

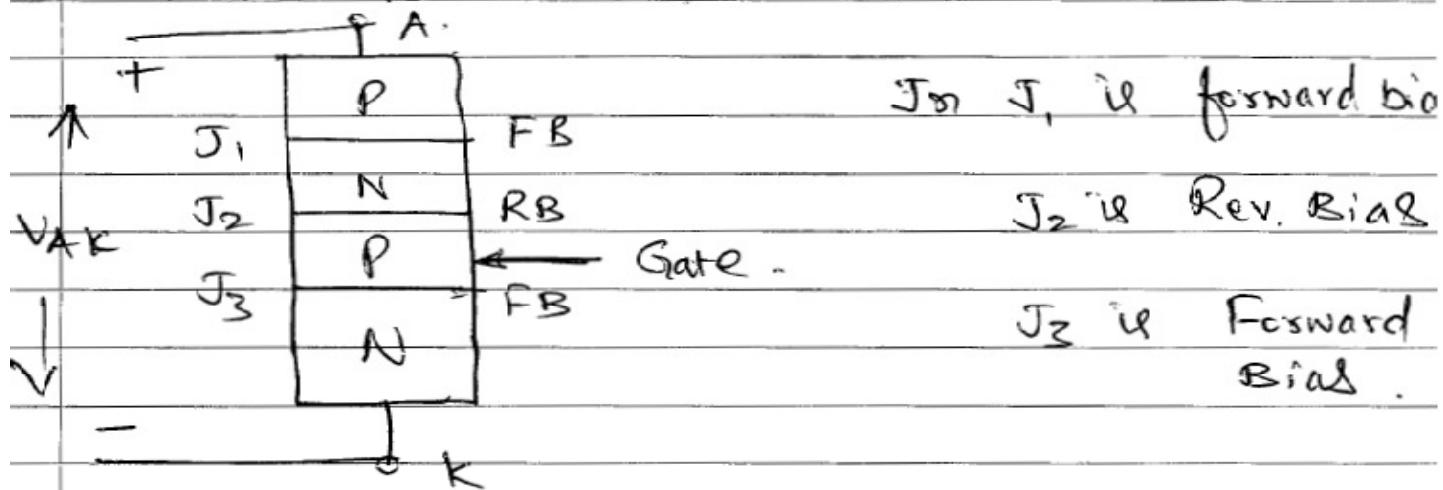Under forward bias condition that is when Anode is supplied with +ve volt and Cathode to -ve.



As V_{AK} anode to cathode voltage is applied conduction of SCR will not take place as J₂ is reverse biased.



Increasing of V_{AK} will cause Avalanche breakdown of J₂ which is called as Specified V_{BO} of the device or Break over Voltage of the device.

However making the device to have break over will cause damage to J₂. Hence providing gate cur will cause an avalanche breakdown due to gate cur.

This will be V_{BR} < V_{BO}. This break over is reversible and regenerative making SCR to conduct.

STATIC ANODE AND CATHODE CHARACTERISTICS

VL - CHARACTERISTIC.

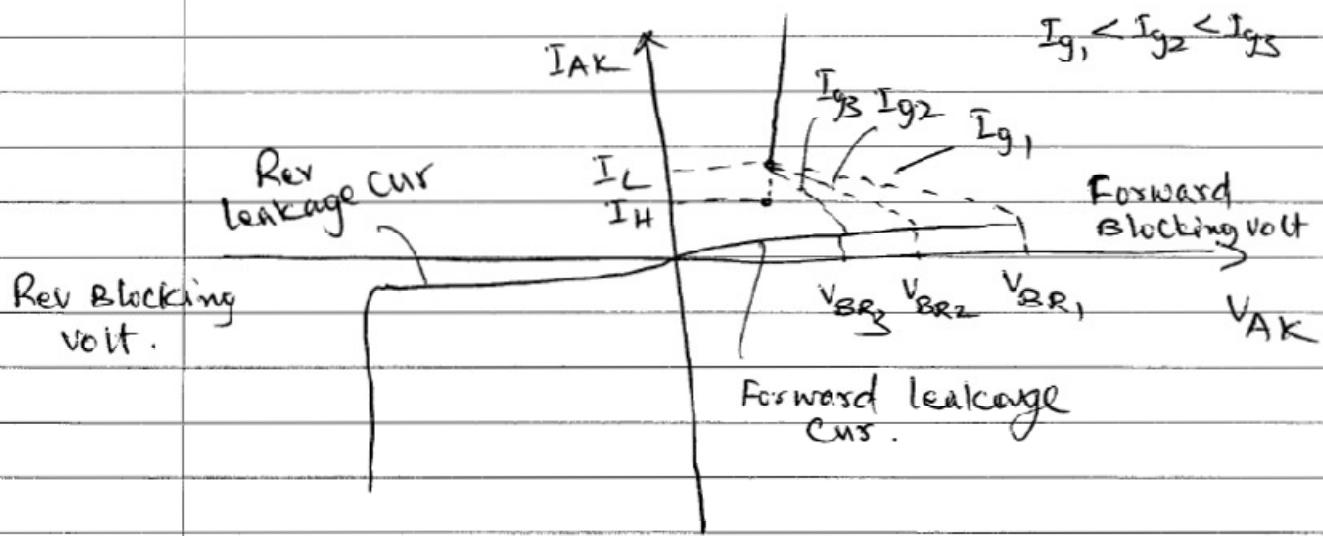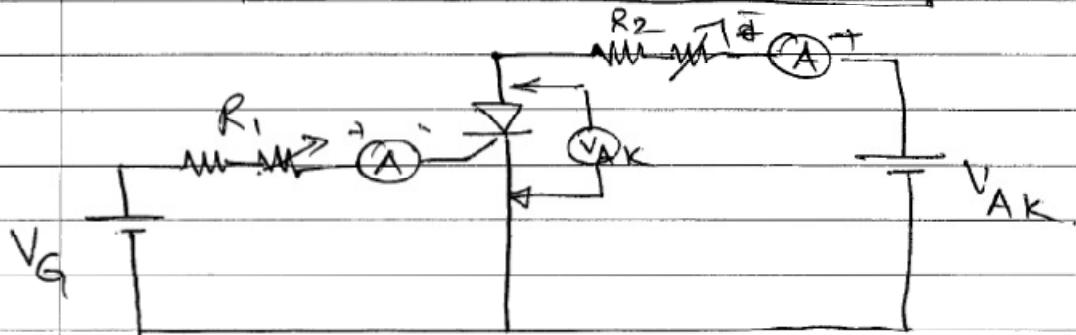

Rev Bias

Forward Bias

Forward Bias

- For a given I_g when V_{AK} is increased

there is a small curr due to J_2 reverse bias condition which is forward leakage curr.

- SCR will block V_{AK} till V_{BR}

(Forward blocking voltage)

3. ~~anode~~ Once $V_{AK} > V_{BR}$; Junction J_2 will have avalanche breakdown hence I_{AK} jumps to a higher cur.

Note: At this time if $I_{AK} < I_L$ and gate cur is removed device will l/n off.


4. The device I_{AK} will continue to increase as V_{AK} is increased and volt across SCR is a small value or $< 1V$

5. Latching cur.: It is the minimum anode current required to keep the SCR in ON-state, while switching on even if gate current is not there or zero.

6. Holding cur.: It is the minimum anode current required for device to be ON while in conduction. If anode cur goes below holding cur the SCR will turn off.
Reverse bias:

1. The device characteristic is similar to diode reverse characteristic. with J_1 & J_3 junctions reverse biased and J_2 forward biased.

TWO TRANSISTOR ANALOGY

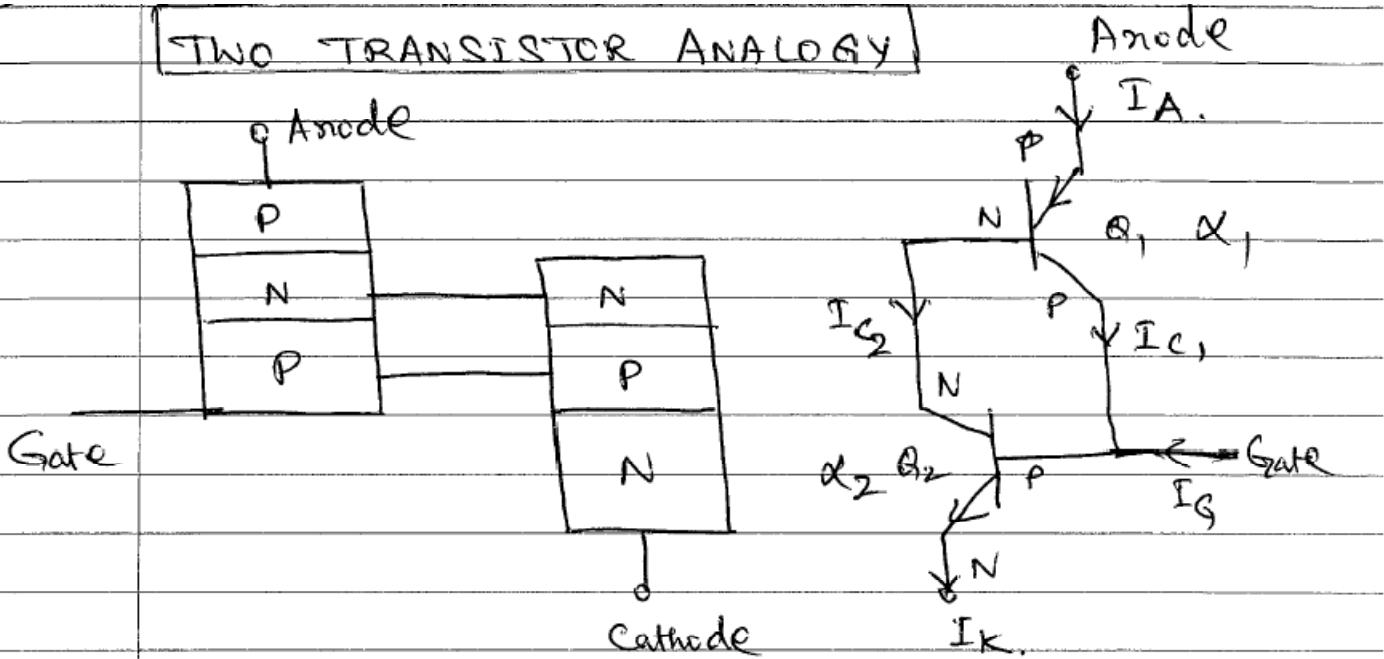

Case 1 In a transistor :

$$I_C = \alpha I_E + I_{CO}$$

$$\text{In } Q_1. \quad I_{C1} = \alpha_1 I_A + I_{CO1} \quad \therefore I_{E1} = I_A$$

$$\text{In } Q_2 \quad I_{C2} = \alpha_2 I_K + I_{CO2} \quad \therefore I_{E2} = I_K.$$

$$\text{TOTAL Anode Curr: } I_A = I_{C1} + I_{C2}$$

$$\therefore I_A = \alpha_1 I_A + \alpha_2 I_K + I_{CO1} + I_{CO2}$$

$$\boxed{I_A = \alpha_1 I_A + \alpha_2 I_K + I_{CO}} \quad - ①$$

$$\text{where } I_{CO1} + I_{CO2} = I_{CO}.$$

Case - 1 \therefore When $I_G = 0$

$$I_A = I_K$$

\therefore Eqn ① will be.

$$I_A = \alpha_1 I_A + \alpha_2 I_A + I_{CO} = I_A (\alpha_1 + \alpha_2) + I_C$$

$$\text{or } I_A (1 - (\alpha_1 + \alpha_2)) = I_{CO}$$

or
$$I_A = \frac{I_{CO}}{1 - (\alpha_1 + \alpha_2)}$$
 — ②

Case-2: When $I_G \neq 0 \therefore I_K = I_A + I_G$

\therefore Eqn ① will be.

$$I_A = \alpha_1 I_A + \alpha_2 (I_A + I_G) + I_{CO}$$

or
$$I_A = \frac{\alpha_2 I_G + I_{CO}}{1 - (\alpha_1 + \alpha_2)}$$
 — ③

Hence it can be observed that small I_G can cause large I_A .

GATE CHARACTERISTICS

The SCR Conduction is controlled by gate current. A safe operating region, which would ensure successful switching on of the SCR so also not causing any damage to Gate is defined by Gate characteristics.


Important parameters restricting the operating zone are.

Gate

- (i) Current : Max value & Min value
 $I_{g\max}$ & $I_{g\min}$
- (ii) Gate volt : Max & min value
($V_{g\max}$ & $V_{g\min}$)
- (iii) Temperature : Max and min value.
- (iv) Noise triggering value.

(v) Power distribution

(Continuous &
Pulsed)

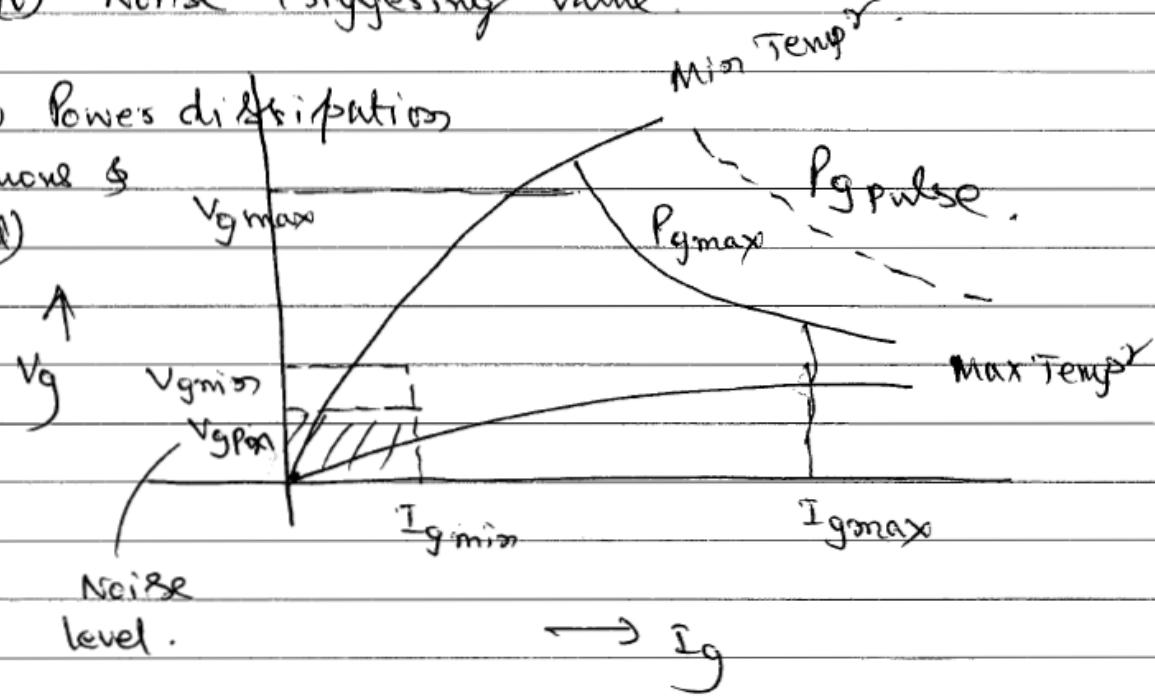

TURN ON METHODS of SCR.

→ 1. Forward Voltage Triggering :

When V_{Ak} Anode to Cathode Voltage is increased more than forward Break over Voltage V_{BO} of SCR, it will have Avalanche breakdown hence SCR turns on.

2. Thermal or Temperature Triggering

Increase in temperature decreased depletion layer
at close to V_{BO} forward break over volt, increase
in junction temperature \Rightarrow caused SCR to turn on

3. Radiation or Light Triggering

In SCRs like LASCR, external radiation or light causes more number of electron-hole pair to be created. Eventually causing SCR to turn on.

4. $\frac{dV}{dt}$ Triggering :

A sudden increase in Anode to Cathode voltage can trigger SCR to switch on.

$$i_c = \frac{dQ}{dt} \quad \text{where } Q \text{ is the charge.}$$

$$= \frac{d(C_j V)}{dt} \quad C_j = J_{DS} \text{ Capacitance.}$$

$$i_c = V \frac{dC_j}{dt} + C_j \frac{dv}{dt}$$

As $\frac{dC_j}{dt}$ rate of change of J_{DS} capacitance is very small:

$i_c \approx C_j \frac{dv}{dt}$ \therefore Sudden increase in voltage can trigger the SCR.

5. GATE TRIGGERING.)

Most popular and Commonly used method.

(i) DC Gate Triggering: A Continuous DC Supply provides the required gate current for SCR to switch ON.

This method suffers lack of isolation and both power & control circuits are DC.

(ii) AC Gate Triggering: A step down AC is applied to the gate to provide gate current during Positive cycles.

This method provides isolation as transformer is present but at the same time increased power loss and cost of the circuit.

(iii) Pulse gate triggering :

Most popular technique used for triggering the SCR.

In this a single pulse appears multiple times so that SCR will turn ON and power dissipation requirement is also less.

This method provides isolation between high current and control circuit.

Further loss in gate circuit is also less.

~~STUDY~~

NOTE:


REFER PPT FOR MORE EXPLANATION.

P-11

DYNAMIC TURN ON CHARACTERISTICS

SWITCHING CH OF SCR.

1. Switching on Characteristics.

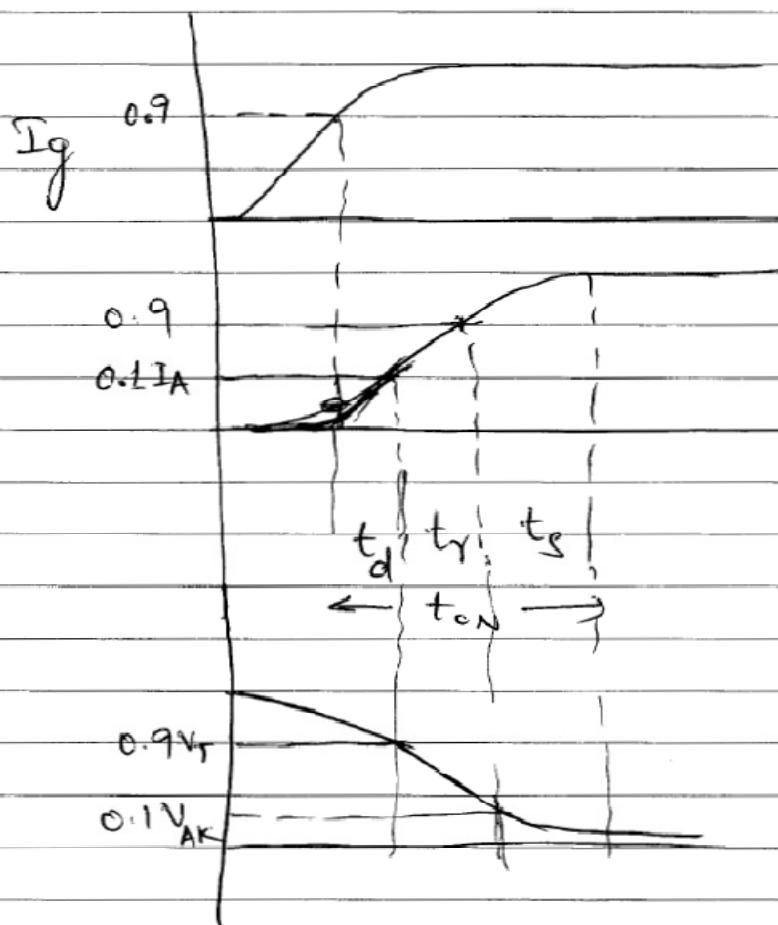

$$t_{ON} = t_d + t_r + t_s$$

where $t_d \Rightarrow$ delay time: Time taken by I_{AK} to reach 10% of final value.

The delay is due to the conduction limited to gate and cathode.


$t_r \Rightarrow$ rise time: Time taken by output reach from 10% to 90% of final value.

→ This is attributable to load inductor and value and rate of increase in TAK.

$t_s \Rightarrow$ Spread time: Time taken by output current to reach final value from 90%.

→ This is the time taken by the current to spread on complete Cathode area. Depends on surface area and the current value.

TURN OFF CHARACTERISTICS

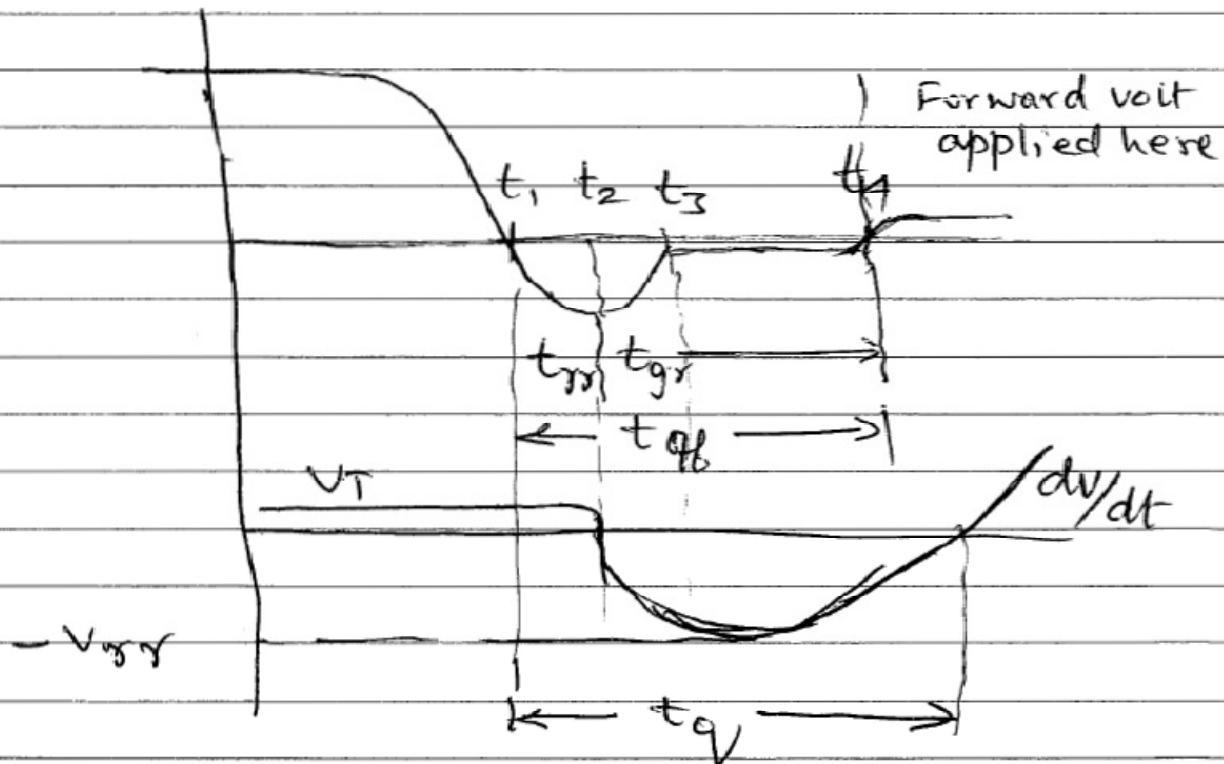

$$t_{off} = t_{rr} + t_{gs}$$

$t_{rr} \rightarrow$ reverse recovery time: Time taken by excessive carriers to settle back

$t_{gs} \rightarrow$ reverse gate recovery time.

- Time taken by trapped charges to recombine and settle back.

$t_g \Rightarrow$ switch off time which includes gate recovery due to reverse induced voltage V_{RR} (reverse recovery voltage)

$t_c \rightarrow$ circuit time. (Swing time of the circuit.)

$$t_c > t_g$$

Note $V_{RR} < V_{RM}$ (reverse volt of SCR specified by manufacturer)

[TURN OFF METHODS]

Commutation means change of current path.

In thyristor it is used to signify that the current from one thyristor is changed to other. But this is not possible unless the current is made zero in the thyristor.

Circuit used for reducing the current

~~below the holding cur is known as
Turn off method or Commutation
Circuit.~~

Methods of Commutation :

Natural

↓
OR

Line Commutation.

↓

Use the i/p AC voltage
to naturally reduce
the SCR current in
one cycle.

Forced

↓

An external
commutation circ
is used to turn
off the thyristor.

CLASS A COMMUTATION :

by resonating the load.

OR.


LC Commutation:

OR CURRENT Commutation :


An LC circuit is used to resonate
and reduce the SCR current below
holding current.

I method : Load in parallel.

II method : Load in series.

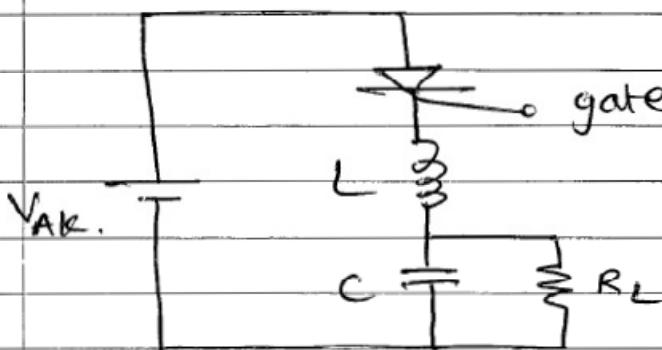

Load is \parallel led to Capacitor.

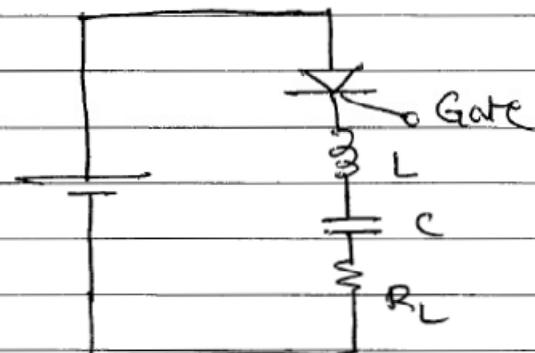


Load is Series with Capacitor.

Features :-


1. LC tank Circuit is used
2. Cap can be in \parallel or \perp series to load
3. Commutation or S/W off of SCR is due to reduction of current below the holding cur.

Hence can be termed as Current Commutation also.


Current wave form in LC circuit

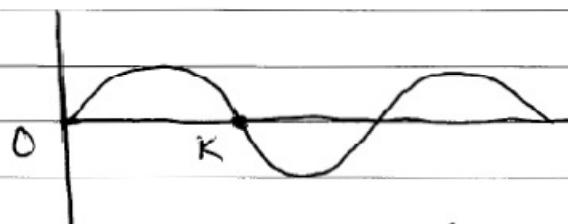

Current wave form for RLC series config

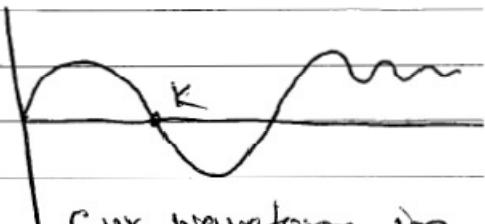

Cur waveform in \parallel led config.

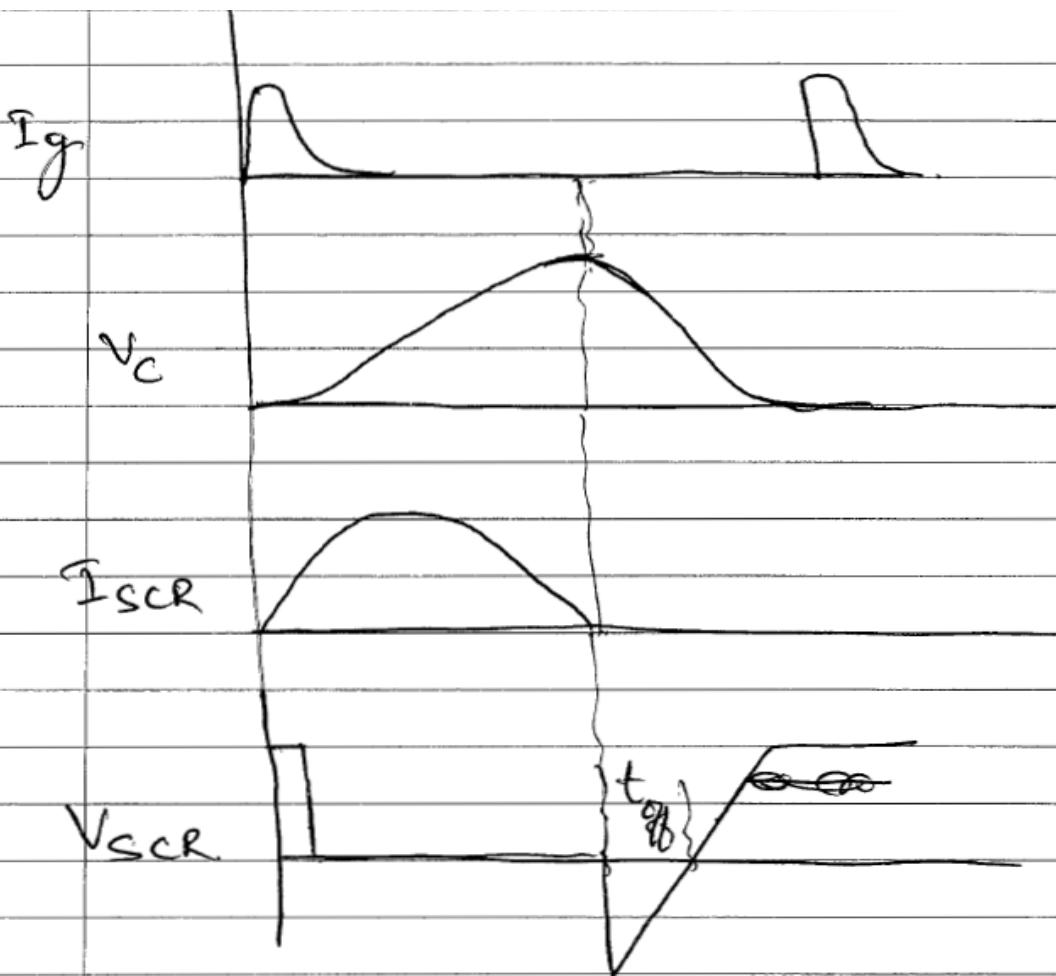

DESIGN CONSIDERATIONS :

When R_L is in parallel to Capacitor.

$$E_{dc} = L \frac{di}{dt} + v \quad \text{where } v = v \text{ across load}$$

$$i(t) = C \frac{dv}{dt} + \frac{v}{R}$$

Taking Laplace transform

$$E_{dc}(s) = I(s)LS + V(s)$$

$$I(s) = CSV(s) + \frac{V(s)}{R}$$

$$V(s) = E_{dc}(s) - LS I(s)$$

$$I(s) = \left(Cs + \frac{1}{R} \right) [E_{dc}(s) - LS I(s)]$$

$$I(s) \otimes \left[1 + LS \left(Cs + \frac{1}{R} \right) \right] = E_{dc}(s) \left[Cs + \frac{1}{R} \right]$$

$$I(s) = \frac{E_{dc}}{s} \frac{(Rcs + 1)}{R + RLCs^2 + LS}$$

$$I(s) = \frac{E_{dc} (1 + Rcs)}{s (RLC) (s^2 + \frac{1}{RC}s + \frac{1}{LC})}$$

which is a second order system and by partial fraction and taking laplace inverse

$$i(t) = \frac{E_{dc}}{R} \left[1 + \frac{\omega_n^2}{\xi \sqrt{1 - \xi^2}} e^{-t/RC} \sin(\omega t + \phi) \right]$$

$$\text{where } \omega_n = \frac{1}{\sqrt{LC}} \quad \xi = \frac{1}{2 * \frac{1}{\sqrt{LC}}} = \frac{1}{2R} \sqrt{\frac{L}{C}}$$

$$\omega = \omega_n \sqrt{1 - \xi^2} = \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{L}{4R^2C}} =$$


$$\omega = \sqrt{\frac{1}{LC} - \frac{1}{4R^2C^2}}$$

$$\phi = \tan^{-1} 2RC\omega$$

$$V(s) = \frac{E_{dc}}{LC \left(s^2 + \frac{1}{RC}s + \frac{1}{LC} \right)}$$



$$V(t) = E_{dc} \frac{\omega_0}{\sqrt{1-\xi^2}} e^{-t/\tau_{02}^2 RC} \left[\sin \omega t + \frac{E_{dc}}{\omega_0} \right]$$

EXPRESSION FOR SERIES RLC CONFIGURATION

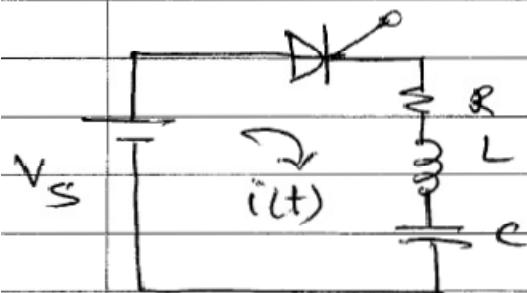

Conditions under which SCR turns off are

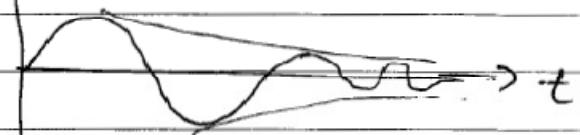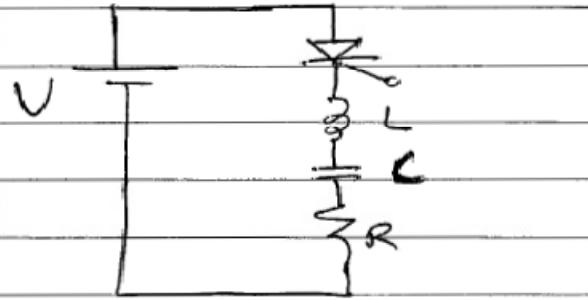- (i) When biasing the SCR becomes zero.
- (ii) When reverse bias is applied externally across the SCR.
- (iii) When external current pulse is forced in reverse direction.
- (iv) Resonating load, which reverse biases the SCR.



$$\text{By KVL} \quad V = i(t)R + L \frac{di}{dt} + \frac{1}{C} \int i(t) dt$$

$$= \frac{V}{s} = I(s)R + LS I(s) + \frac{1}{Cs} [I(s) + CV_0]$$

where $CV_0 = \text{Cap due to initial charge}$

If $V_0 = 0$ no charge in Cap initially then
 $CV_0 = 0$,

$$\therefore \frac{V}{s} = \frac{I(s)}{Cs} [R(s + LCs^2 + 1)] + \frac{V_0}{s}$$

$$I(s) = \frac{\frac{V}{s} - \frac{V_0}{s}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Roots of denominator : $s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$

$$s_{1,2} = -\frac{R}{2L} \pm j\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

$$= -\xi\omega_n \pm j\sqrt{(1-\xi^2)}\omega_n$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = s^2 + 2\zeta\omega_n s + \omega_n^2$$

$$= (s + \zeta\omega_n)^2 + \omega_d^2$$

where $\omega_n = \frac{1}{\sqrt{LC}}$ $\zeta = \frac{R}{2L} \cdot \frac{1}{\sqrt{LC}} = \frac{R}{2\sqrt{LC}}$

$$\zeta\omega_n = \frac{R}{2L} \quad \omega_d = \omega_n \sqrt{1 - \zeta^2}$$

$$\omega_d = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

$$I(s) = \frac{\frac{V}{L} - \frac{V_0}{L}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{\frac{V}{L} - \frac{V_0}{L}}{(s + \zeta\omega_n)^2 + \omega_d^2}$$

$$I(s) = \frac{V - V_0}{\omega_d L} \left[\frac{\omega_d}{(s + \zeta\omega_n)^2 + \omega_d^2} \right]$$

$$i(t) = \frac{V - V_0}{\omega_d L} e^{-\zeta\omega_n t} \sin \omega_d t$$

Current $i(t)$ reached natural zero

$$\text{when } \omega_d t_0 = \pi \text{ or } t_0 = \frac{\pi}{\omega_d}$$

$$\text{or } t_0 = \frac{1}{\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}}$$

For System to be underdamped is C_{ns} to decay exponentially

$$\omega_d > 0$$

$$\therefore \frac{1}{LC} - \frac{R^2}{4L^2} > 0$$

$$\text{or } R < \sqrt{\frac{4L}{C}}$$

Voltage across Capacitor.

Case - 1 : When $V_0 = 0$ i.e. no initial charge on Capacitor.

$$V_C = V - V_L = V - L \frac{di}{dt}$$

$$V_C(t) = \frac{V}{e^{-\zeta \omega_n t}} \sin \omega_d t$$

$$\frac{di}{dt} = \frac{V}{\omega_d L} \left[-\zeta \omega_n e^{-\zeta \omega_n t} \sin \omega_d t + e^{(-\zeta \omega_n t)} \cos \omega_d t \right]$$

$$\cos \pi = -1 \quad \sin \pi = 0$$

Max voltage across Cap is when

$$w_d t = \pi .$$

$$\therefore \frac{di}{dt} = \frac{v}{w_d L} \left[0 - e^{-\zeta w_n \frac{\pi}{w_d}} \right]$$

$$= -\frac{v}{L} e^{-\zeta w_n}$$

$$\therefore V_c = v - L \frac{di}{dt} = v + L * \frac{v}{L} e^{-\zeta w_n}$$

$$V_c = v \left[1 + e^{-\zeta w_n} \right]$$

If $V_0 \neq 0$


Then V_c ~~is a damped oscillation~~

$$V_c = v + (v - V_0) e^{-\zeta w_n}$$

CLASS-B


SELF COMMUTATION

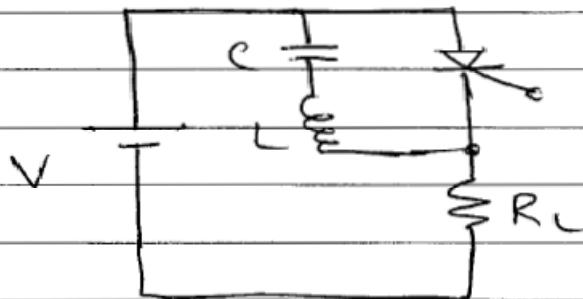- This type of Commutation is used in chopper and inverter circuits.
- In Class A load cur passes through L and C.
- ii. Commutating Components take load cur
- In Class B load cur is independent of LC Components




Operations

Case-1: When SCR off . STAGE-1

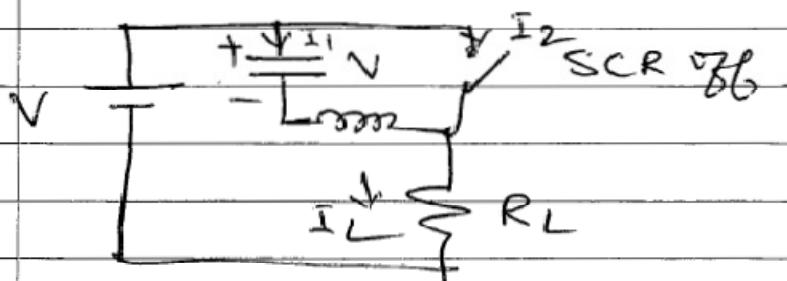

$$I_L = I_1 \quad I_{SCR} = I_1 + I_2 \quad I_2 = 0$$

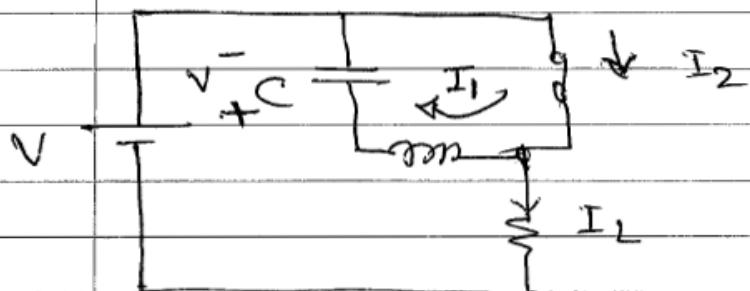
Stage-2: When SCR is ON (triggered from Stage-1)



$$I_L = I_1 + I_2$$

$$I_{SCR} = I_L$$

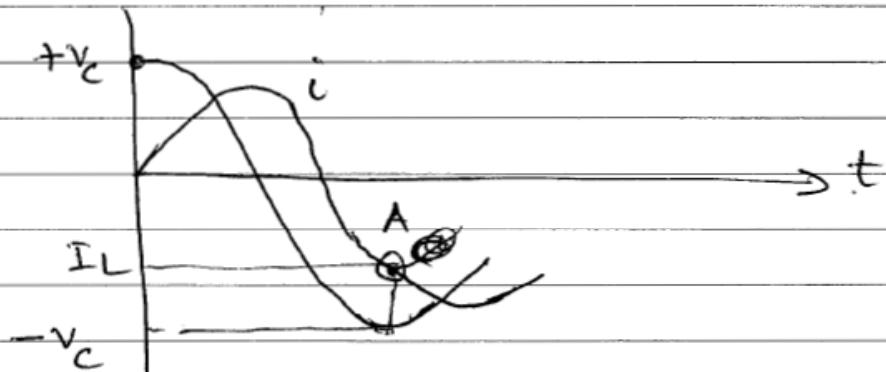
Cap charges from $+V_C$ to $-V_C$ or $+V$ to $-V$.




$$\text{At } A \quad I_1 = I_2$$

once Cap charges to $-V$ $I_1 = 0$ & reversed direction making $I_{SCR} = I_2 - I_1$

Stage 3:

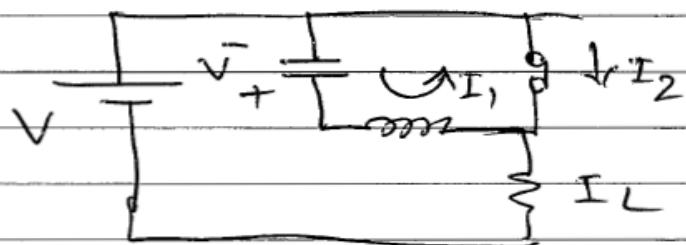

$$I_{SCR} = I_2 - I_1$$

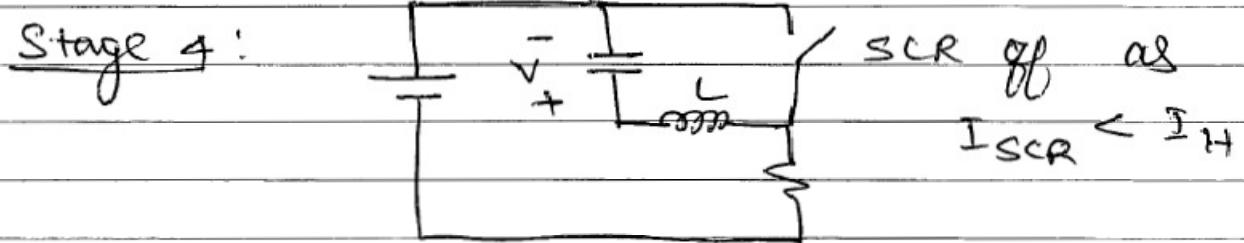

Stage 5 Back to Stage 1.

This is continuous so that SCR is turned on and off continuously. RC product controls the time of S/W on and off.

DESIGN CONSIDERATION

Consider the LC circuit i.e. eqⁿ for I_1 (loop of LC & SCR)

$$L \frac{di}{dt} + \frac{1}{C} \int i(t) dt = V$$

By Laplace Transform

$$\frac{V}{s} = \left[Ls + \frac{1}{Cs} \right] I(s)$$

$$\text{or } I(s) = \frac{\frac{V}{s}}{L \left(s^2 + \frac{1}{LC} \right)} = \frac{\frac{V}{s}}{\left(s^2 + \frac{1}{LC} \right)}$$

$$I(s) = \frac{\frac{V}{s}}{s^2 + \left(\frac{1}{\sqrt{LC}} \right)^2} = \frac{\frac{V}{s}}{\frac{1}{\sqrt{LC}}} * \frac{\frac{1}{\sqrt{LC}}}{s^2 + \left(\frac{1}{\sqrt{LC}} \right)^2}$$

Taking laplace inverse of the same.

$$i(t) = V \sqrt{\frac{C}{L}} \sin w_n t$$

where $w_n = \frac{1}{\sqrt{LC}}$.

∴ $i(t)$ is a sinusoidal variation.

Voltage across Capacitor.

$$V_C = V - L \frac{di}{dt}$$

$$= V - L * V * \sqrt{\frac{C}{L}} (\cos w_n t) * w_n$$

$$= V - V \sqrt{\frac{C}{L}} * \frac{1}{\sqrt{LC}} \cos w_n t$$

$$V_C = V [1 - \cos w_n t]$$

Peak Cur $I_{peak} = I_m = V \sqrt{\frac{C}{L}}$

$$= 2 I_L$$

at least double the load cur or when $I_1 = I_2$

or $\textcircled{Q} = 2 I_1 = 2 I_2 = 2 I_L$

Commutating time is taken as $\frac{1}{4}$ of
the period of sinusoidal voltage or 2π

$$\therefore \omega_m t = \frac{\pi}{2}$$


$$\text{or } t = \frac{\pi}{2} \times \sqrt{LC}$$

~~Show ZL~~

P-29

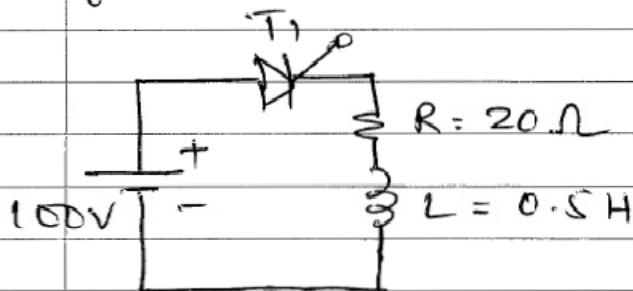PROBLEMS

Prob ①: The latching circuit of a thyristor is shown. Circuit is 50mA. The duration of firing pulse is 5ms will the thyristor get fired and continue to be on.



$$\text{By KVL} \quad V = i(t)R + L \frac{di}{dt}$$

$$\text{By Laplace transform} \quad \frac{V}{s} = (R + LS) I(s)$$

$$\text{or } I(s) = \frac{\frac{V}{s}}{L(s + \frac{R}{L})} = \frac{V/L}{s(s + R/L)}$$

$$\text{By Partial fraction } I(s) = \frac{A}{s} + \frac{B}{s + R/L}$$

$$\text{or } \frac{V}{L} = A(s + R/L) + BS$$

$$\text{Let } s=0: \quad \frac{V}{L} = A \frac{R}{L} \text{ or } A = \frac{V}{R}$$

$$\text{Let } s = -R/L \quad \frac{V}{L} = -B \frac{R}{L} \quad B = -\frac{V}{R}$$

$$\text{or } I(s) = \frac{V}{R} \frac{1}{s} - \frac{V}{R} \frac{1}{s + R/L}$$

~~Stamp 2~~

By Laplace inverse.

$$i(t) = \frac{V}{R} (1 - e^{-t/R})$$


$$\therefore i(t) = \frac{100}{20} (1 - e^{-\frac{t}{20}})$$

$t = 50\mu s$

$$= 9.99 \text{ mA} \approx [10 \text{ mA}]$$

The SCR will be on only for the duration of gate pulse and then off as Anode cur is 10mA at $50\mu s <$ Latching cur.

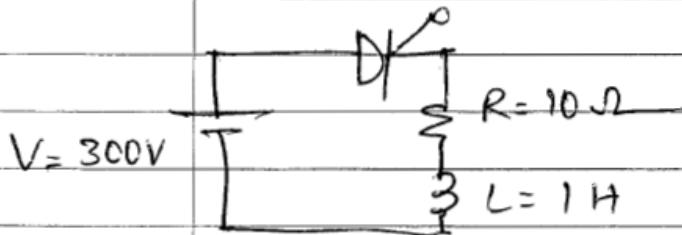Prob ②. The SCR has latching cur of 25mA if fired by the gate pulse width of 60μs Find state of SCR



⑥ Find the trigger pulse width if latching cur is 10mA

P-31

~~Ans 3)~~

$$\text{Ans: Part A} \quad i(t) = \frac{V}{R} (1 - e^{-\frac{t}{R/L}})$$

$$i(t) = \frac{300}{10} (1 - e^{-\frac{60 \times 10^{-6} t}{10}})$$

$$t = 60 \mu s$$

$$i(t) = 17 \text{ mA} \quad \text{which is } < I_L = 25 \text{ mA}$$

Hence SCR is off.


$$\text{Part B: } i(t) = I_L = 10 \times 10 = \frac{300}{10} (1 - e^{-\frac{t}{10}})$$

$$= [t = \dots \text{ msec.}]$$

Prob ③: The thyristor is triggered by pulse width of 40μs and latching cur is 36 mA for a load of 60Ω in series with 2H induct

Will the thyristor remain ON, if not then how it can be overcome. The supply voltage V 220V.

Ans: Ckt:

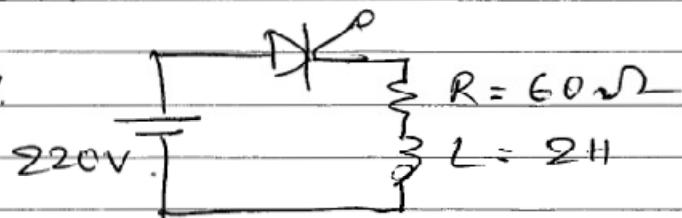

$$i(t) = \frac{V}{R} (1 - e^{-\frac{Rt}{L}})$$

~~Ans 2)~~

$$= 40 \times 10^{-6} \times 60$$

$$i(t) = \frac{220}{60} (1 - e^{-\frac{t}{2}})$$

$$(i(t)) = 4.397 \text{ mA} < I_L$$

$$t = 40 \mu\text{s}$$

∴ SCR is off after $40 \mu\text{s}$.

Part B :

$$i(t) = I_L = 36 \times 10^{-3} = \frac{V}{R} (1 - e^{-\frac{t}{R/L}})$$

$$= 36 \times 10^{-3} = \frac{220}{60} \left(1 - e^{-\frac{t \times 60}{2}}\right)$$

$$t = 0.329 \text{ msec}$$


$$\text{or } [329 \mu\text{sec}]$$

Increase the gate trigger pulse width
to $329 \mu\text{s}$ from $40 \mu\text{s}$.

Prob 4): The input volt is $325 \sin \omega t$
for a thyristor with latching curr I_L
 $= 15 \text{ mA}$ and a load of 10Ω with
 0.1 H inductor. Obtain the gate trigger
pulse width for the SCR to be on
at $\pi/6$ angle of the half cycle.

~~Prob 2)~~

Ans:

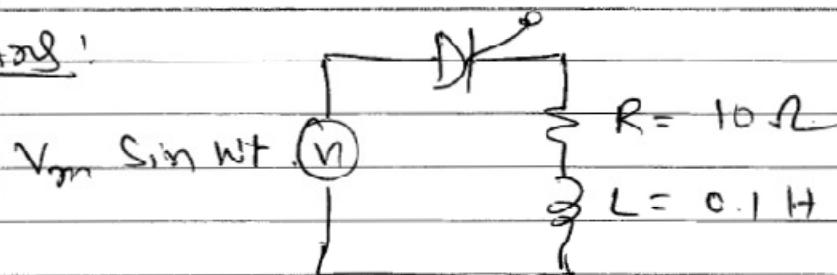

$$\text{At } \omega t = \pi/6, \quad V_{im} = 325 \sin \pi/6$$

$$V_{im} = 162.5 \text{ V}$$

$$i(t) = I_L = \frac{V_{im}}{R} (1 - e^{-t \frac{R}{L}})$$

$$= 15 * 10^{-3} = \frac{162.5}{10} (1 - e^{-t \frac{10}{0.1}})$$

$$t = 9.23 \mu\text{sec}$$

Prob 5): Same Prob 4) with $R = 20 \Omega$

$$L = 0.5 \text{ H} \quad V_{im} = 325 \sin \omega t$$

$$I_L = 20 \text{ mA} \quad \text{firing } \omega = \pi/3$$

$$\text{Ans: } V_{im} = 325 \sin \pi/3 = 281.45 \text{ V.}$$


$$i(t) = I_L = \frac{V_{im}}{R} (1 - e^{-t \frac{R}{L}})$$

$$20 \times 10^{-3} = \frac{281.45}{20} (1 - e^{-\frac{t}{0.5}})$$

$$\boxed{t = 0.355 \mu\text{sec}}$$

→ 0 →

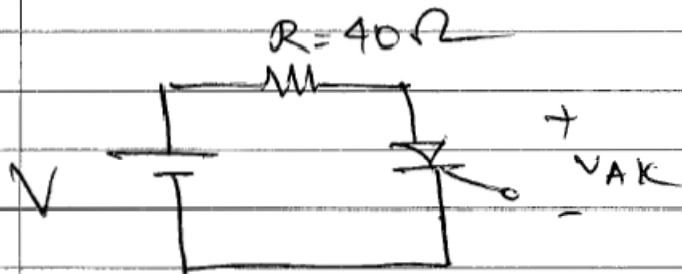Prob ⑥: The on state volt drop across SCR is 0.8V. The thyristor has a holding cur of 15mA with $I_g = 0$. If SCR is turned on by a momentary gate pulse find the voltage value below which SCR will turn off.



$$\text{By KVL } V = i(t)R + V_{AK}$$

$$i(t) = \frac{V - V_{AK}}{R}$$


if $i(t) < I_H$ SCR will turn off

$$\therefore \frac{V - V_{AK}}{R} \leq I_H \text{ for turning off.}$$

$$\therefore \boxed{V \leq 1.4 \text{ V.}}$$

Prob(7): If the Capacitance of the reverse biased junction J2 of SCR $C_{J2} = 30 \text{ pF}$

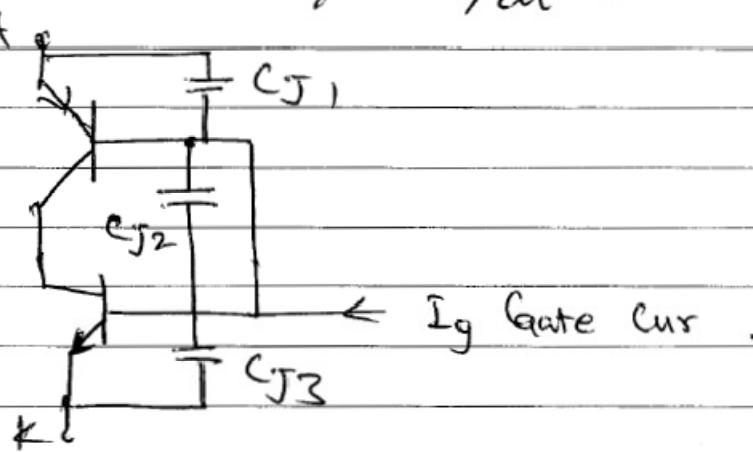assuming it to be independent of off state voltage and the limiting value of charging current to turn ON SCR is 12 mA calculate the critical value of dV/dt .



$$i_{J2} = \frac{d(q_{J2})}{dt} = \frac{d(C_{J2}V)}{dt} = C_{J2} \frac{dv}{dt} + V \frac{dc_{J2}}{dt}$$

$\frac{dc_{J2}}{dt}$ is very small and may be neglected.

$$\therefore i_{J2} = C_{J2} \frac{dv}{dt}$$

$$\therefore \frac{dv}{dt} = \frac{i_{J2}}{C_{J2}} = \frac{12 \times 10^{-3}}{30 \times 10^{-12}} = 400 \times 10^6 \text{ V/s}$$

or
$$\boxed{\frac{dv}{dt} = 400 \text{ V}/\mu\text{sec}}$$


Prob ⑧: The limiting value of charging cur to turn on the SCR is 5mA . If the critical value of $\frac{dv_Ak}{dt}$ is $200\text{V}/\mu\text{Sec}$

Calculate for Capacitance.

From previous prob.

$$C_j = \frac{i_{j2}}{\frac{dv}{dt}} = \frac{5 \times 10^{-3}}{200 \times 10^6} = 25\text{pF.}$$

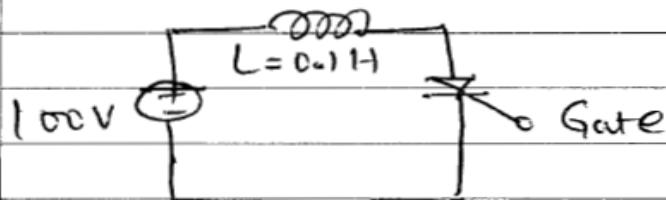Prob ⑨: If the latching cur in the circuit shown is 4mA obtain the minimum width of the gating pulse required to properly turn on the SCR.



By KVL $L \frac{di}{dt} = V$ Neglecting V_{SCE} while on.

$$L \frac{di}{dt} = V dt$$

$$\text{By } \int^{i(t)}_0 L i(t) = V t$$


$$\text{or } t = \frac{L}{V} i(t)$$

$$t = \frac{0.1}{100} \xrightarrow{-3} 4 \times 10^{-6} = \boxed{4 \mu\text{Sec}}$$

Prob 10: In certain thyristor circuit the initial rate of rise of anode cur is $4000 \text{ A}/\mu\text{sec}$. Find the min width of the gate pulse required to turn on the SCR if latching cur is 20mA .

$$\frac{di}{dt} = \frac{I_L}{t_p}$$

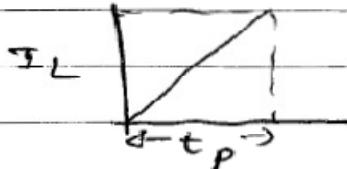
$$\therefore t_p = \frac{20 * 10^{-3}}{4000 * 10^{-6}} =$$



Neglecting
 t_d & t_s

$$t_p = 5 \mu\text{sec.}$$

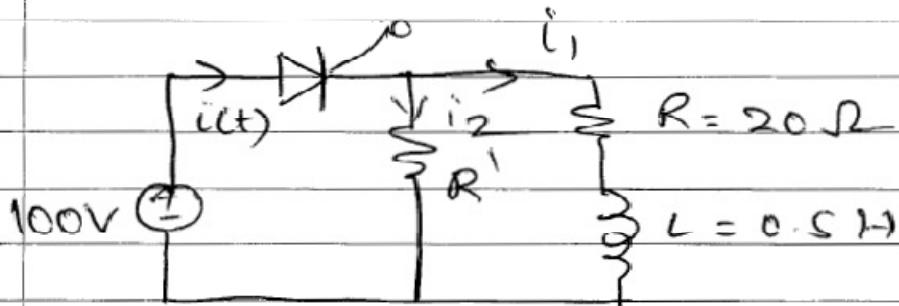Prob 11. The thyristor in circuit has a latching cur of 50mA and is triggered by gate pulse width $50\mu\text{s}$. Show that without resistance R' the thyristor will fail to remain ON, when gating pulse ends. Also find maximum value of R' to ensure firing of SCR. The on state volt across SCR may be neglected.



$$i(t) = i_1 = \frac{V}{R} (1 - e^{-t R/L})$$

$$t = 50 \mu\text{s}$$

~~8 Am 4/1~~

$$-\frac{50 \times 10^{-6} \times 20}{20}$$

$$i_A(t) = \frac{100}{20} (1 - e^{-0.5})$$

Without R'

$$= \underline{10 \text{ mA}} < I_L$$

$$i_2 = C_{\text{bus}} \text{ ths}' R' = i(t) - i_1(t)$$

$$= I_L - i_1(t)$$

$$= 50 \text{ mA} - 10 \text{ mA} = 40 \text{ mA}$$

$$\therefore R' = \frac{V}{i_2(t)} = \frac{100}{40 \text{ mA}} = \boxed{2.5 \text{ k}\Omega}$$

$$\therefore R' \leq 2.5 \text{ k}\Omega \text{ to make } i(t) \geq I_L$$

Prob 12: A thyristor has forward break over voltage of 175V when a pulse of 2mA is made to flow. Find conduction angle if sinusoidal $V_S = 350 \text{ V}$ peak is applied

$$V_S = 350 \sin \omega t$$

$$\text{or } 350 \sin \alpha = 175$$

$$\text{or } \alpha = \sin^{-1} \frac{175}{350} = 30^\circ \text{ or } \pi/6$$

REFER PPT FOR MORE PROBS

PROBLEMS ON COMMUTATION

1 In a half wave rectifier circuit thru off time of SCR is $20\ \mu\text{sec}$. $V = 100\text{V}$ Sinw

Find whether line or natural commutation is possible in following cases.

$$(a) \omega = 100\pi; \alpha = 0 \quad R = 5\Omega$$

$$(b) \omega = 100\pi; \alpha = \pi/2 \quad R = 5\Omega$$

$$(c) \omega = 100 \times 10^3 \pi; \alpha = 0; R = 5\Omega$$

Ans: (a) $\omega = 100\pi$ or $f = \frac{100\pi}{2\pi} = 50\text{Hz}$

$$T = \frac{1}{f} = 20\text{ mSecs.}$$

$$\therefore T/2 \text{ } \frac{1}{2} \text{ cycle time} = [10\text{ mSecs}]$$

t_{off} of SCR = $20\ \mu\text{sec}$ \therefore SCR will be off commutation is successful.

Case-2 $\therefore \alpha = \pi/2 \therefore$ off time is 10 mSecs and 5 mSecs from the cycle.

Commutation is successful.

Case-3: $W = 100 \times 10^3 \times \pi$

$$\text{or } f = 50 \text{ kHz}$$

$$\text{or } T = 20 \mu\text{sec.}$$

$$\frac{1}{2} \text{ cycle time} = \frac{T}{2} = 10 \mu\text{sec.}$$

$$t_{off} = 20 \mu\text{sec.}$$

$\therefore T/2 < t_{off}$ hence SCR will not turn off completely.

Commutation fails

VTU 2002: Compare Natural and forced commutation.

SL No.	Parameter	Natural Commutation	Forced Commutation
1.	Need of Commutating Components	Nil	Necessary
2.	Type of Supply	AC	DC
3.	Power loss in Commutating Ckt	Nil	Yes
4.	Type of Commutation	$I_A < I_H$ as V_{AK} is reversed	Cus or volt commutation

5	Cost of Commutation Ckt	Nil	Costly
6	Size of Circuit	Small	Big.

VTU Aug 2002

Compare Volt & Cur Commutation Ckt


VOLTAGE

CURRENT

- | | |
|---|---|
| 1. Turned off due to -ve V_{AK} . | 1. Turned off at $I_A < I_H$ |
| 2. A charged Capacitor is placed across SCR | 2. A Cap is discharged thr' SCR |
| 3. Line Commutation is Volt Commutation | 3. Natural Commutation is Cur Commutation |
| 4. Complementary or Aux or impulse. | Self Commutation or Resonant Pulse |

VTU Mar 03 6mks

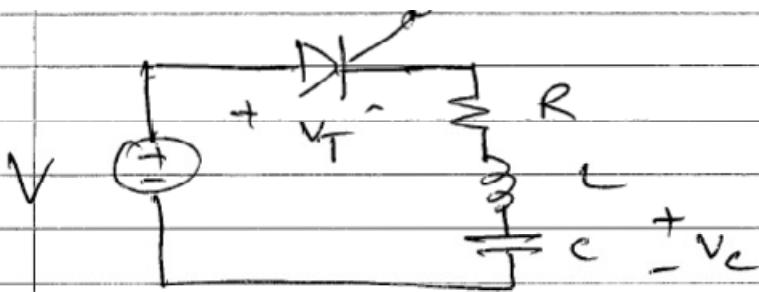Prob ①: In the load Commutation Circuit shown in fig has $R = 10\Omega$ $L = 10\text{mH}$ $C = 10\text{MF}$, $V = 100\text{V}$ determine whether thyristor will be self commutated or not If it is commutated calculate volt across capacitor at that time.



For Commutation to be successful.

$$w_d t_0 = \bar{\lambda}$$

$$\text{or } t_0 = \frac{\bar{\lambda}}{w_d} = \frac{\bar{\lambda}}{\sqrt{\frac{1}{2C} - \frac{R^2}{4L^2}}}$$

$$t_0 = 1.006 * 10^{-3} \text{ sec}$$

$$V_c = V \left[1 + e^{-\frac{\bar{\lambda} w_d}{R}} \right]$$

$$= V \left[1 + e^{-\frac{\bar{\lambda} R}{2L} \sqrt{\frac{1}{2C} - \frac{R^2}{4L^2}}} \right]$$

$$V_c = 160.463 \text{ V}$$

Prob ②: In the previous problem if Cap is charged to $-500 \text{ V} = V_c(0)$

$$L = 15 \mu\text{H} \text{ and } C = 50 \mu\text{F} \text{ and } R = 0$$

and SCR turned on at $t=0$ find

(a) Peak value of resonant cur.

(b) Conduction time of thyristors.

Ans: If Cap is Charged initially.

$$i(t) = \frac{V - V_0}{\frac{w_d L}{C}} e^{-\frac{w_m t}{w_d L}} \sin w_d t$$

SCR is ON at $t=0$, and $V=0$

$$\therefore i(t) \Big|_{t=0} = -\frac{V_0}{w_d L} \sin w_d t$$

$i(t)$ is max when $X_C = X_L$ or $w_d = w_m = \frac{1}{\sqrt{LC}}$

and $w_m t = \pi/2$

$$i(t) \Big|_{\text{Peak}} = -\frac{V_0}{w_m L} = -V_0 \sqrt{\frac{C}{L}}$$

$$= -\frac{500}{\sqrt{15 \times 10^{-6}}} * \sqrt{50 \times 10^6}$$

$$\left(i(t) \right)_{\text{Peak}} = \boxed{912.87 \text{ A.}}$$

Conduction time of SCR is $C_{UR} = 0$.
 $t=0$ SCR starts conducting till C_{UR} becomes zero again.

$$\therefore \omega_m t = \pi \text{ makes } i(t) = 0.$$

$$\therefore t = \frac{\pi}{\omega_m} = \pi \sqrt{LC}$$

$$t = 86.04 \mu s$$

Prob ③: A thyristor commutation circuit has commutating elements L & C in series with load resistance R

$$\text{If } R = 0.8 \Omega, L = 10 \mu H, C = 50 \mu F$$

Check that the circuit is underdamped and thyristor conduction time.

Ans: In Series RLC Commutation Circuit for system to be underdamped.

$$R < \sqrt{\frac{4L}{C}} \text{ or } \omega_d > 0$$

$$\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} > 0$$

$$\therefore R < 0.8944 \Omega$$

Given $R = 0.8 \Omega$ hence Condition for Underdamping is satisfied.

For Conduction time $\omega_d t_0 = \pi$

$$\text{or } t_0 = \frac{\pi}{\omega_d} = \frac{\pi}{\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}}$$

$$t_0 = 157.08 \mu\text{sec}$$

SCR Commutates when $t = t_0$ or conduct till t_0 .

Prob ④: In a self commutating circuit load cur is 8A Supply volt is 90V and required turn off time is 40μS

Find values L & C of the Commutation clt.

$$\text{Ans: Assume } I_{\text{peak}} = 2 I_L$$

SCR rev biased for $\frac{1}{4}$ of total time period

$$I_{\text{peak}} = V \sqrt{\frac{C}{L}} = 2 I_L = 16$$

$$= 90 \sqrt{\frac{C}{L}} = 16 \text{ or } \sqrt{\frac{C}{L}} = \frac{16}{90} \quad \text{---(1)}$$

$$\omega_n t = \frac{\pi}{2} = t_c$$

$$\text{or } t = \frac{\pi}{2} * \frac{1}{\omega_n} = \frac{\pi}{2} \sqrt{LC} = 40 * 10^{-6}$$

As $t_c = 40 \mu\text{sec}$.

$$\therefore \boxed{\sqrt{LC} = \frac{80 * 10^{-6}}{\pi}} - \textcircled{2}$$

By multiplying ① & ②.

$$\boxed{C = 4.522 * 10^{-6} \text{ F}}$$

By dividing ① & ②

$$\boxed{L = 143.24 * 10^{-6} \text{ H.}}$$

— o —

~~Ques 21:~~

TRIGGERING CIRCUITS

Need : The gate cur and voltage of SCR needs to be within limits as seen in gate characteristics.

Further duration of gate trigger must be such that the anode cur of SCR will be at least or more than latching current if not the SCR will not be in ON condition.

Hence a separate triggering circuit is required for SCR.


TRIGGERING CIRCUITS :

1. R Triggering Ckt

2. RC Triggering Ckt

3. UJT Triggering Ckt.


1. R - TRIGGERING CIRCUIT

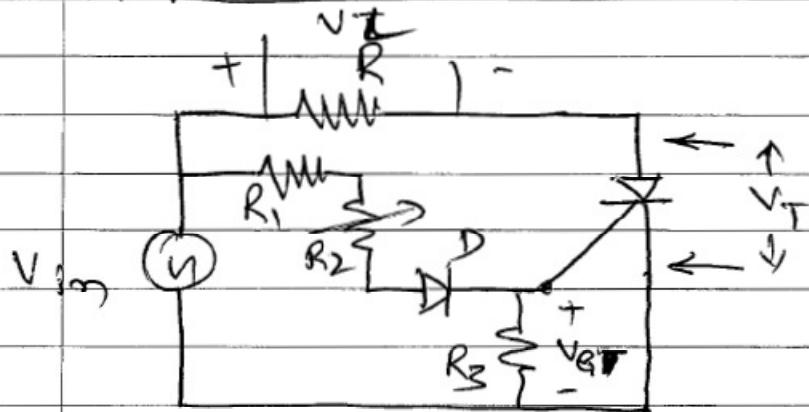

OPERATION / WORKING.

1. I/P is a Sine wave or V_m Sin wt
2. Based on R_2 value gate cur I_g varies which will influence the triggering or conducting voltage V_{AK} or V_{SCR} .
3. More R_2 value less is I_g more if V_{AK} reqd for SCR to conduct.
4. Diode D steps reverse cur from SCR to gate crt.

waveform:

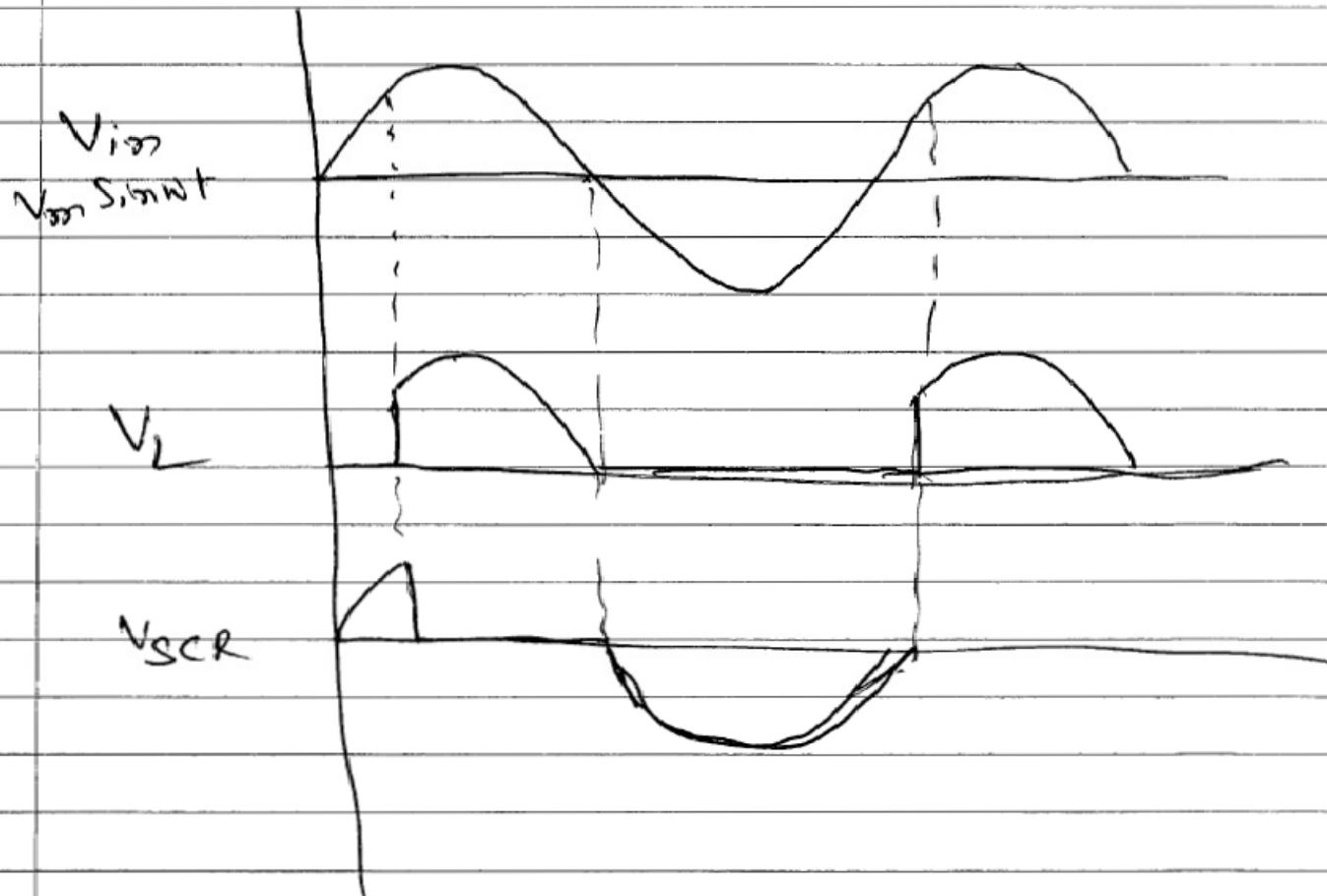

DESIGN CONSIDERATION

$$1. \frac{V_m}{R_1 + R_2} = \frac{V_m}{R_1} \leq I_{Gm}$$

Max when

$$R_2 = 0$$

I_{Gm} max gate cur \downarrow
device or SCR

$$\therefore \boxed{R_1 \geq \frac{V_m}{I_{Gm}}} \quad - ①$$

$$2. \frac{V_m * R_3}{R_1 + R_3} \leq V_{Gm} \quad \text{where } V_{Gm} \text{ is}$$

\downarrow
max gate volt
device or SCR

$$\therefore \boxed{R_3 \leq \frac{V_m R_1}{V_m - V_{Gm}}} \quad - ②$$


3. SCR fires when

$$V_{GP} \sin \alpha = V_{GT}$$

$$\text{or } \alpha = \sin^{-1} \frac{V_{GT}}{V_{GP}}$$

$$= \sin^{-1} \frac{V_{GT}}{\frac{V_m * R_3}{R_1 + R_2 + R_3}}$$
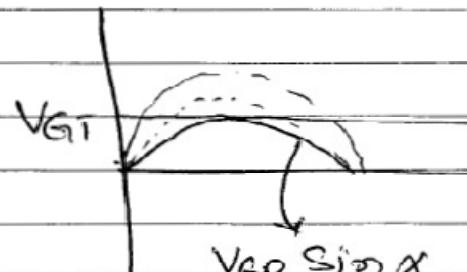
$$\alpha = \sin^{-1} \frac{V_{GT} (R_1 + R_2 + R_3)}{V_m R_3}$$



$$\begin{aligned} V_{GP} &= \text{volt drop across } R_3 \\ &= \frac{V_m R_3}{R_1 + R_2 + R_3} \end{aligned}$$

Instantaneous volt at the time of conduction

$$V = I_{GT} (R_1 + R_2) + V_g + V_{GT}$$

where I_{GT} gate triggering cur

V_{GT} Gate triggering volt

V_g Drop across Diode D.


Main Disadvantage of R triggering is that

Max Firing Line $\alpha < 90^\circ$


RC TRIGGERING CIRCUIT.

Half wave rectifier Configuration,

Circuit:

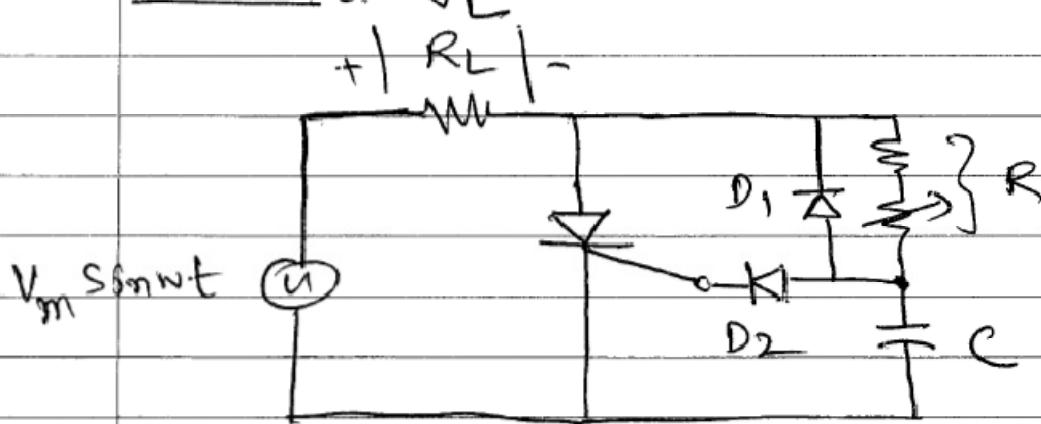

wave forms :-

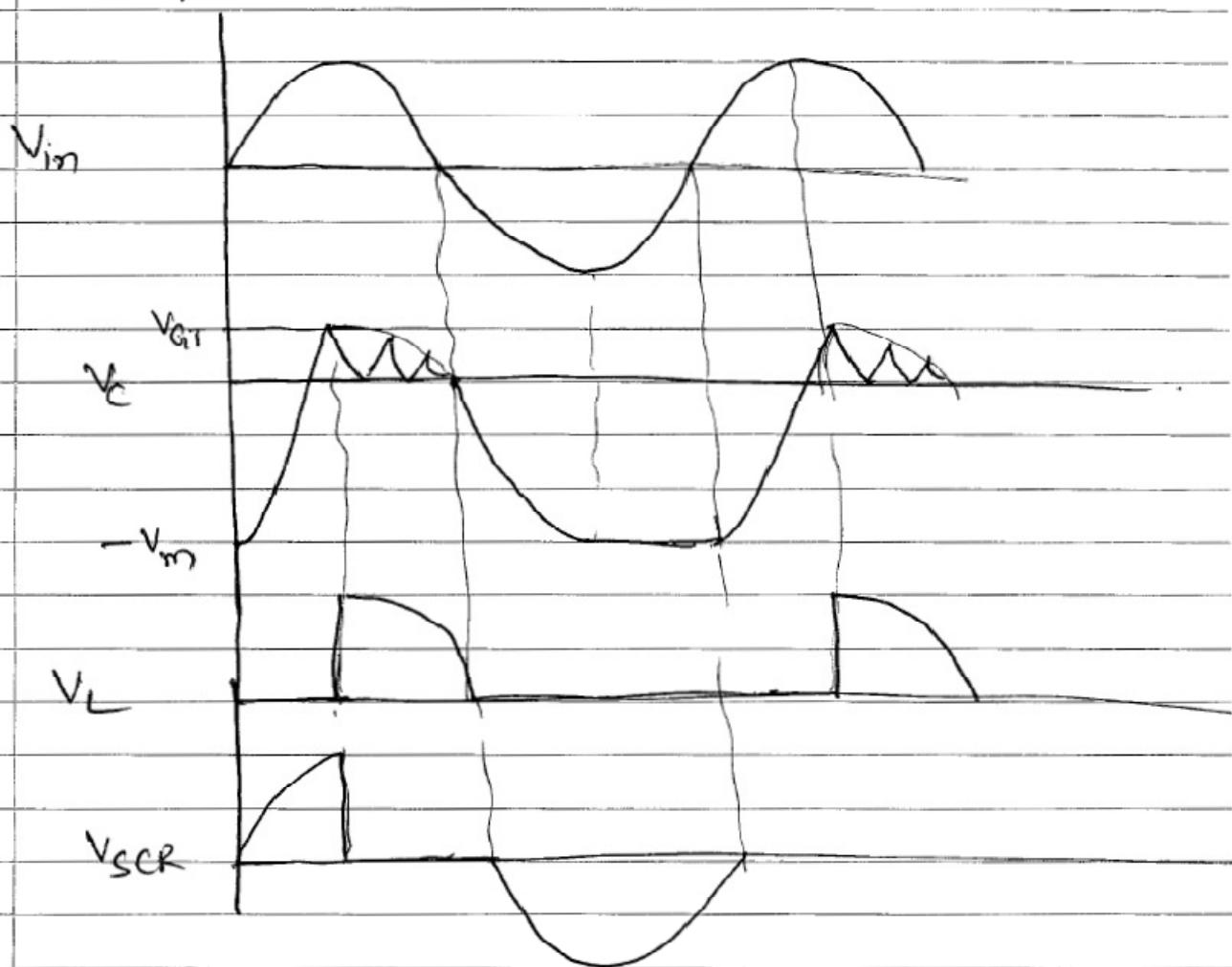

Working:- Cap C gets charged to $-V_m$ during
-ve half cycle thr' diode D₁


- Cap C charged to $+V_m$ during the half
cycle and before it reached V_{os} based
on the V_{GT} Diode D₂ is forward biased
and trigger SCR.

- The Cap Charging time during the half


cycle is controlled by RC time constant.

Half time of firing of SCR depends on R value.

~~DESI~~ FULL WAVE CONFIGURATION

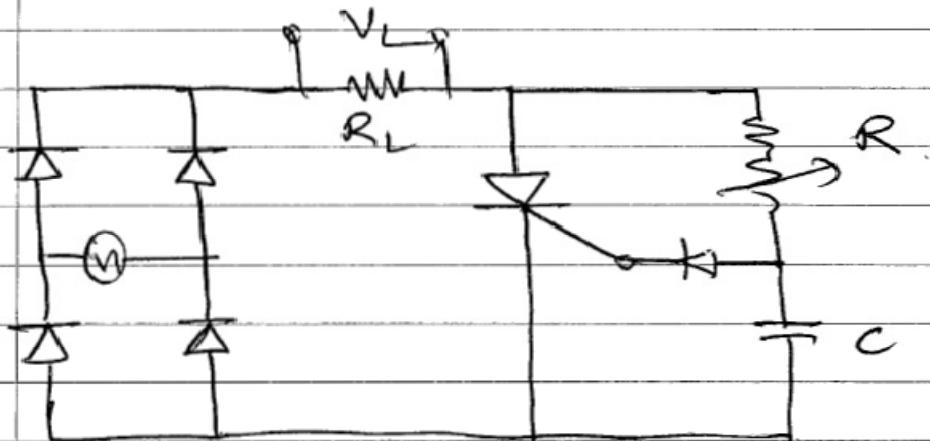

waveforms:

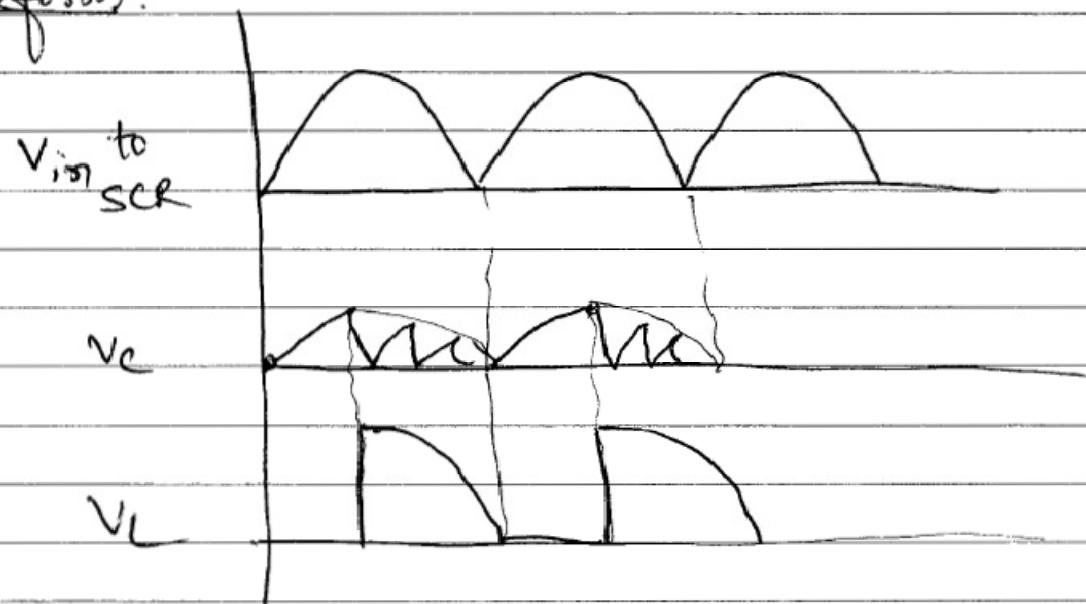

The Capacitor is charged thro' R in every half cycle. The SCR fires based on anode ~~cur~~ voltage and corresponding gate cur.

DESIGN EQUATIONS :

HN Configuration $RC \geq \frac{10^3}{2} T$

FW Configuration $RC \geq 25 T$

where T is operating time period.


$$R = R_1 + R_2 = \frac{V - V_{GT} - V_r}{I_{gt}} \quad \text{HN Config}$$

$$R = R_1 + R_2 = \frac{V - V_{GT}}{I_{ignition}} \quad \text{FW Config.}$$


UJT TRIGGERING CKT.

INTRODUCTION TO UJT


SYMBOL

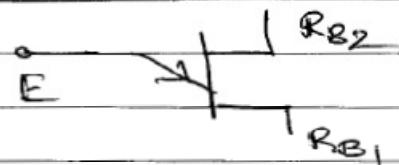

CONSTRUCTION

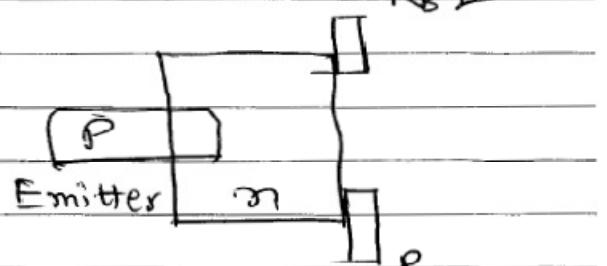

Equivalent :

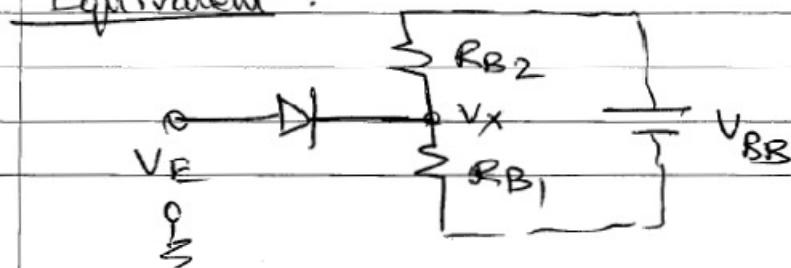

$$V_x = \frac{R_{B1}}{R_{B1} + R_{B2}} V_{BB}$$

R_{B1} , Metallic contact

$$V_x = \eta V_{BB} \quad \text{where } \eta = \frac{R_{B1}}{R_{B1} + R_{B2}}$$


Intrinsic Stand off ratio (η)

≈ 0.5 to 0.82


e. For UJT to Conduct $V_E \geq \eta V_{BB} + V_r$

$$\boxed{V_E \geq V_p}$$

Ch of UJT ?

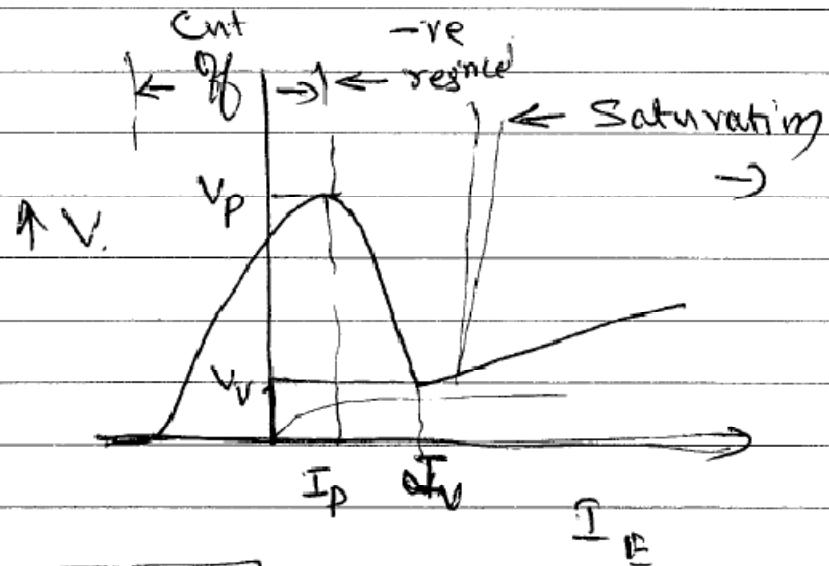

UJT Triggering Circuit.

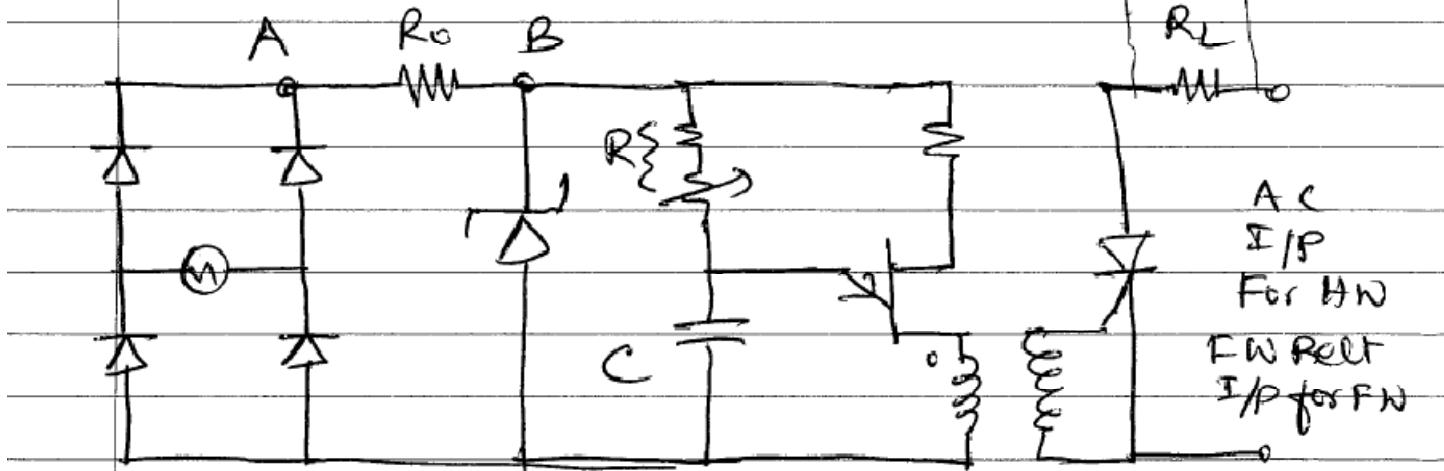

Waveforms:

AC
I/P


Pt A

Pt B

V_C

V_L
HN Config

V_L
FN Config

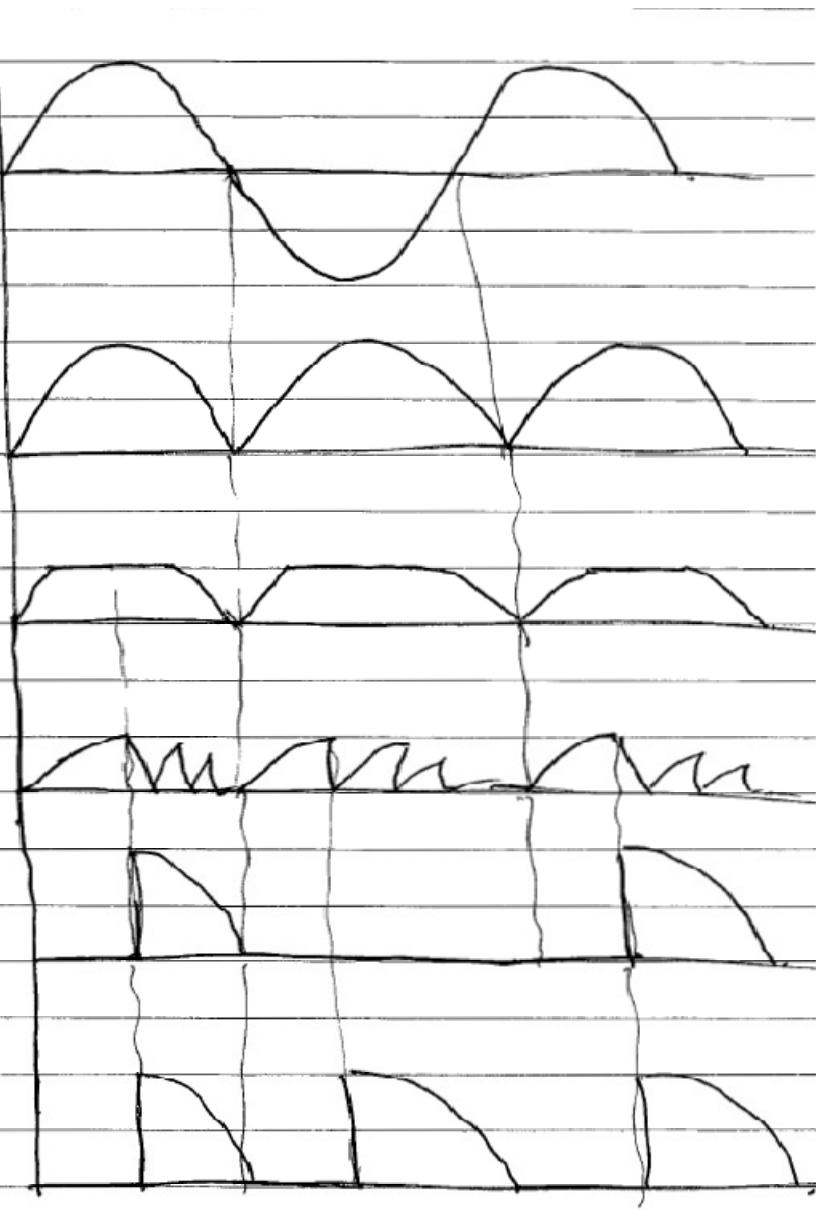


Working:

1. FW rectifier Supplies FW rectified signal to V_Z or Zener.
2. Zener diode regulates Current thru it to Const Volt i/p for RC Ckt for linear Control.
3. Based on RC Value Cap Charges to V_m

4. At some time $V_C \geq V_P$ the UJT Conducts a trigger through pulse transformer if given to gate of SCR.
5. Based on H/W or F/W I/P to SCR O/P across load will be controlled rectified output.

DESIGN CONSIDERATION

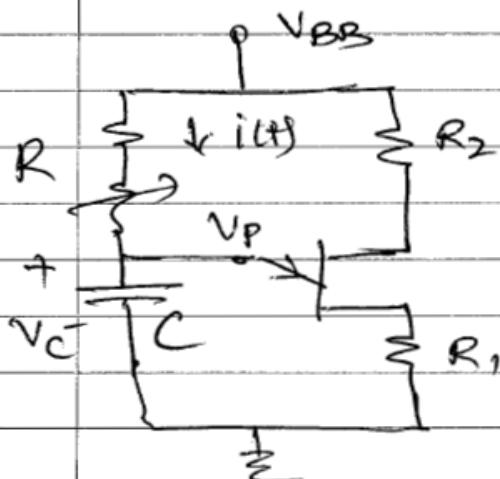

When UJT is off or cap charging time

By KVL

$$V_{BB} = i(+R + \frac{1}{C} \int i(t) dt)$$

Take Laplace Tfm.

$$\frac{V_{BB}}{S} = (R + \frac{1}{CS}) \oplus I(s)$$

$$\text{or } I(s) = \frac{\frac{V_{BB}}{S}}{R}$$

$$\left(s + \frac{1}{RC} \right)$$

$$\mathcal{L}^{-1} \left\{ i(t) = \frac{V_{BB}}{R} e^{-t/RC} \right\} \quad \text{--- (1)}$$

$$\text{At any given time, } V_C = V_{BB} - i(t)R$$

$$V_C = V_{BB} - \frac{V_{BB}}{R} e^{-t/RC} \neq R$$

~~Slowly~~

$$\text{So } V_C = V_{BB} \left(1 - e^{-\frac{t}{RC}} \right) \quad - \textcircled{2}$$

For UJT to conduct $V_C \geq V_p \approx V_{BB}$

$$\text{So } V_{BB} \left(1 - e^{-\frac{T}{RC}} \right) = V_{BB} \quad \text{where } T \text{ is the time of UJT turning on.}$$

$$\text{So } T = RC \ln \frac{1}{1-\eta} \quad - \textcircled{3}$$

R_{max} & R_{min} Design.

For UJT to be off

$$V_C = V_{BB} - I_p R_{max} \geq V_p$$

$$\text{or } R_{max} \leq \frac{V_{BB} - V_p}{I_p} \quad - \textcircled{4}$$

$$V_C = V_{BB} - I_v R_{min} \leq V_v \quad \text{For UJT to be off}$$

$$\text{or } R_{min} \geq \frac{V_{BB} - V_v}{I_v} \quad - \textcircled{5}$$

$$R_2 = \frac{0.7 (R_{B1} + R_{B2})}{V_{BB}} \approx \frac{10^4}{V_{BB}} \quad - \textcircled{5}$$

Design of R_1

There are three methods

$$1. R_1 \frac{I_{\text{Leakage}}}{I_{\text{discharge}}} < V_{gmin}$$

$$\therefore R_1 < \frac{V_{gmin}}{I_{\text{discharge}}}$$

$$2. V_{BB} = I_{\text{Leakage}} (R_1 + R_2 + R_{B1} + R_{B2})$$

$$\text{or } R_1 = \frac{V_{BB}}{I_{\text{Leakage}}} - R_2 - R_{B1} - R_{B2}$$

$$3. R_1 C \geq t_g$$

or $5R_1 C \geq t_g$ if Safety factor is considered.

t_g = gate trigger Pulse width.

Freq of UJT :

$$f_{\text{max}} = \frac{1}{T_{\text{min}}} = \frac{1}{R_{\text{min}} C \ln \frac{1}{1-\eta}}$$

$$f_{\text{min}} = \frac{1}{T_{\text{max}}} = \frac{1}{R_{\text{max}} C \ln \frac{1}{1-\eta}}$$

$$\text{Firing Lle of UJT} = \omega T = (2\pi f) \times R C \ln \frac{1}{1-\eta}$$

~~8/10/21~~

PROBLEMS OF
TRIGGERING CIRCUITS

Prob ①: In R triggering circuit gate voltage required to trigger SCR is $V_{GT} = 0.6\text{V}$ and corresponding gate cur is $I_{GT} = 250\mu\text{A}$

The material used for diode is Silicon and input volt is $U = 100 \sin \omega t$. Find firing angle if $R_1 = 10\text{k}\Omega$ & $R_2 = 220\text{k}\Omega$

Ans:

$$V_D = 0.7\text{V} \text{ as Si diode}$$

$$U = I_{GT} (R_1 + R_2) + V_{GT} + V_D$$

$$= 250 * 10^{-6} (10 + 220) * 10 + 0.6 + 0.7$$

$$\boxed{U = 58.8\text{V}}$$

$$U = U_m \sin \alpha = 100 \sin \alpha = 58.8$$

$$\alpha = \sin^{-1} \frac{58.8}{100} = 36.01^\circ$$

$\therefore \boxed{\text{SCR fired at } 36.01^\circ}$

Prob ②: For the R triggering circuit firing angle required is 60° . If the input is $100 \sin \omega t$ find the value of resistor R_2 when $R_1 = 300\text{k}\Omega$, $V_{GT} = 0.8\text{V}$, $I_{GT} = 200\mu\text{A}$ & diode is of Germanium.

$$\checkmark \text{ Ans: } V_m \sin \omega t = 100 \sin 60^\circ = [86.6 \text{ V}]$$

$$\therefore U = 86.6 = I_{G1}(R_1 + R_2) + V_{G1} + V_Y$$

$$= 200 * 10^{-6} (300 * 10^3 + R_2) + 0.8 + 0.3$$


$$R_1 + R_2 = 427.5 \text{ k}\Omega$$

$$\text{or } R_2 = 127.5 \text{ k}\Omega$$

or 200 kΩ Pot.

| REFER PPT for more Prob. |

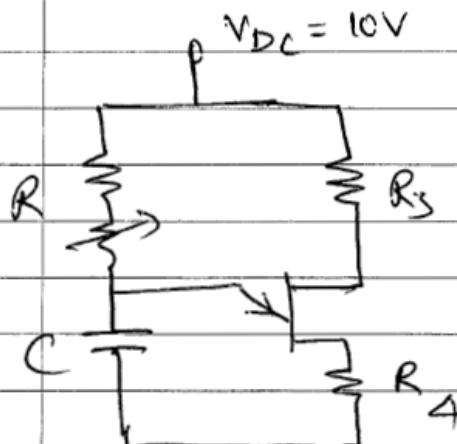Prob(3): A relaxation oscillator is to be designed to generate 2 kHz output. $V_{DC} = 10V$
 $\eta = 0.6$, peak discharge cur 5 mA.
 Neglect discharge time for calculating freq.



$$\text{Assume } V_Y = 0.5 \text{ V}$$

$$V_P = \eta V_{BB} + V_Y$$

$$= 0.6 * 10 + 0.5$$

$$V_P = 6.5 \text{ V.}$$

$$R_{max} \leq \frac{V_{BB} - V_P}{I_P} = \frac{10 - 6.5}{5 * 10^{-3}} \leq 700 \Omega$$

Assume $C = 0.5 \mu F$.

$$\textcircled{B} \quad T = \frac{1}{f} = RC \ln \frac{1}{1-\eta}$$

$$\text{or } R = \frac{1}{fC \ln \frac{1}{1-\eta}} = \underline{\underline{2400 \Omega}}$$
$$= \frac{1}{2 \times 10^3 \times 0.5 \times 10^{-6} \ln \frac{1}{1-0.6}}$$

$$\boxed{R = 1091 \Omega}$$

Note: Permitted $R_{max} < 700 \Omega$
this R value is not acceptable.

Let $C = 1 \mu F$.

$$R = \frac{1}{2 \times 10^3 \times 1 \times 10^{-6} \ln \frac{1}{1-\eta}} = \boxed{545.7 \Omega}$$

Now $R < R_{max}$ hence acceptable.

$$R_3 = \frac{10^4}{27 V_{BB}} = \frac{10^4}{6} \Omega$$

—o—

Prob ④: Design a UJT relaxation oscillator for triggering a thyristor. The UJT has following parameters.

$$\eta = 0.72, I_p = 60 \mu A, V_V = 2.5 V, I_V = 4 mA$$

$V = 15 V$ $R_{BB} = 5 k\Omega$ The leakage current with emitter open is 1 mA .

The triggering freq is 1 kHz and

$V_{gontos} = 0.3 V$. Also find min & max of triggering freq.

Ans: Let $V_T = 0.6 V$ and $C = 0.05 \mu F$.

$$R = \frac{T}{C \ln \frac{1}{1-\eta}} = \frac{1 \times 10^{-3}}{0.05 \times 10^{-6} \ln \frac{1}{1-0.72}}$$

$$R = 15.71 k\Omega$$

$$V_P = \eta V_{BB} + V_T = 0.72 \times 15 + 0.6$$

$$V_P = 11.4 V$$

$$R_{max} \leq \frac{V_{BB} - V_P}{I_P} \leq \frac{15 - 11.4}{60 \times 10^{-6}}$$

$$\leq 60 k\Omega$$

$$R_{\min} \geq \frac{V_{BB} - V_v}{I_N} = \frac{15 - 2.5}{4 \times 10^{-3}} = 3.125 k\Omega$$

$$\geq 3.125 k\Omega$$

$$\therefore R_{\min} < R < R_{\max}$$

$$3.125 k\Omega < 15.71 k\Omega < 60 k\Omega$$

is satisfied.

$$R_2 = 0.7(R_{BB}) \Rightarrow \frac{10^4}{0.7 V_{BB}} = 925.93 \sqrt{2}$$

I method

$$R_1 = \frac{V_{BB}}{I_{leakage}} = R_2 - R_{BB}$$

$$= \frac{15}{1 \times 10^{-3}} - 925.93 - 5 \times 10^3$$

$$R_1 \approx 9 k\Omega$$

$$\text{ii method } \therefore R_1 = \frac{V_{gmin}}{I_{leakage}} = \frac{0.3}{1 \times 10^{-3}} = 300 \Omega$$

$$f_{\min} = \frac{1}{T_{\max}} = 261.86 \text{ Hz}$$

$$f_{\max} = \frac{1}{T_{\min}} = \frac{1}{R_{\min} \times \ln \frac{1}{1-\eta}} = 5.03 \text{ kHz}$$

Prob 5: Design a UJT firing circuit with parameters

$$\eta = 0.66, I_p = 25\mu A, V_V = 2.5V, I_V = 10mA$$

$V = 25V$. The freq of osc³ is 500Hz and width of triggering pulse is 10μs

Assume $V_T = 0.6V$.

Ans: Let $C = 0.1 \mu F$.

$$R = \frac{T}{C \ln \frac{1}{1-\eta}} = \frac{2 \times 10^{-3}}{0.1 \times 10^{-6} \times \ln \frac{1}{1-0.66}}$$

$$R = 18.54 k\Omega$$

$$V_P = \eta V_{BB} + V_T = 0.66 \times 25 + 0.6 = 17.1V$$

$$R_{max} \leq \frac{V_{BB} - V_P}{I_p} = \frac{25 - 17.1}{25 \times 10^{-6}} = 316 k\Omega$$

$$R_{min} \geq \frac{V_{BB} - V_V}{I_V} = \frac{25 - 2.5}{10 \times 10^{-3}} = 2.25 k\Omega$$

$$R_{min} < R < R_{max}$$

$$2.25 k\Omega < 18.54 k\Omega < 316 k\Omega$$

Hence R & C values are acceptable

Step 2: $R_2 = \frac{10^4}{27V_{BE}} = 606.06 \Omega$

Step 3: $5R_1C \geq t_g$.

or $R_1 \geq \frac{t_g}{5C} = 20 \Omega$


$R_1C \geq t_g$ would result $R_1 = 100 \Omega$

Prob ⑥ VTU Aps 99; Aps 96.

A Cap used in UJT osc circuit is charged by Const cur source. The value of the cap is $0.5 \mu F$ and that of the const cur is $1mA$. The saw tooth volt of oscillator is found to have crest value of $8.5V$ and valley level of $2.5V$ calculate freq of oscillator.

Ans: Given $C = 0.5 \mu F$ $i_c = 1mA$ $V_p = 8.5V$ $V_v = 2.5V$
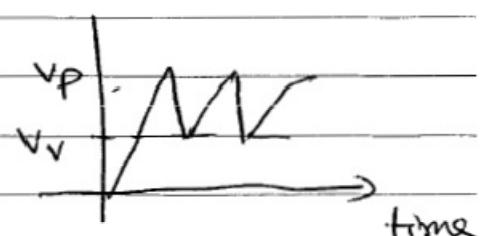
$$V_c = V_p = \frac{1}{C} \int_0^T i(t) dt + V_{c0}$$



$$= \frac{1}{C} i_{\text{const}} \int_0^T dt + V_v$$

Cap Charging

As $i(t)$ is const Charging cur. V_v is the initial volt on capacitor

$$\therefore 8.5 = \frac{1 \times 10}{0.5 \times 10^6} kT + 2.5$$

$$T = 3 \times 10^3 \text{ Sec}$$

$$\text{or } f = \frac{1}{T} = \frac{1}{3} \text{ kHz}$$

Prob ⑦ : Sep Oct 1998 :

A UJT trigger circuit is used to fire a PNPN device. It is supplied from a source across the SCR to be triggered thr' a 10V Zener. Valley and peak volt are 1V and 7V respectively. Calculate intrinsic stand off ratio and freq of oscillator if $R = 1\text{k}\Omega$, $C = 1\mu\text{F}$.

Assume $V_r = 0.8\text{V}$

$$V_p = \eta V_{BR} + V_r$$

$$\therefore \eta = \frac{V_p - V_r}{V_{BR}} = \frac{7 - 0.8}{10} = 0.62$$

$$f = \frac{1}{RC \ln \frac{1}{1-\eta}} = 1.083 \text{ kHz}$$

~~Start~~

Y-07

Max 98 10 mkg

Prob (B): An SCR is to be triggered with UJT
triggering circuit where $\eta = 0.7$, $I_p = 2 \mu A$, $V_p = 16.5 V$

Normal leakage cur with emitter open is 3 mA

$V_V = 1 V$ $I_V = 6 \text{ mA}$, $R_{B1, B2} = 5.5 k\Omega$

triggering freq is 100 Hz. Design the
circuit with $C = 0.1 \mu F$; let $V_g = 0.7 V$.

$$\text{Ans: } R = \frac{1}{f C \ln \frac{1}{1-\eta}} = [83.05 k\Omega]$$

$V_p = \eta V_{BB} + V_V \quad V_{BB} = 22.57$

$$R_{\max} \leftarrow \frac{V_{BB} - V_p}{I_p} = [7.78 M\Omega]$$

$$R_{\min} \leftarrow \frac{V_{BB} - V_V}{I_V} = [3.595 k\Omega]$$

$$\therefore R_{\min} < R < R_{\max}$$

$$3.595 k < 83.05 k < 7.78 M\Omega$$

$\therefore R \& C$ acceptable.

$$R_2 = \frac{10^4}{\eta V_{BB}} = [633 \Omega]$$

$$R_1 = \frac{V_{BB}}{I_{\text{leakage}}} - R_2 - R_{BB} = [1.39 k\Omega]$$

Prob 9: Design a UJT relaxation oscillator for a single phase controlled converter fed from 50 Hz mains. Use 2N2646 UJT whose parameters at Junction temperature of 25°C are as under. Max value of V_{BB} = 35V Max average power dissipation = 300mW. Range of R_{BB} 4.7k Ω to 9.1k Ω (typical value is 5.6k Ω at $V_{BB} = 12\text{V}$) Valley point Cur 4mA

$\eta = 0.56$ to 0.75 with typical value of 0.65
 $V_p = 0.5\text{V}$ valley volt is 2V peak point
 $C_{av}, I_p = 5\text{mA}$ Max volt which will not trigger SCR is 0.18V

Ans: Given $V_{BB} = 12\text{V}$, $R_{BB} = 5.6\text{k}\Omega$, $V_p = 0.5\text{V}$
 $V_V = 2\text{V}$, $I_V = 4\text{mA}$, $I_p = 5\text{mA}$
 $\eta = 0.63$, $V_{trigger} = 0.18\text{V}$.

Design:

(Ans)

$$V_p = \eta V_{BB} + V_V = 0.63 \times 12 + 0.5 = [8.06\text{V}]$$

$$R_{max} \leq \frac{V_{BB} - V_p}{I_p} = \frac{12 - 8.06}{5 \times 10^{-6}} = [788\text{k}\Omega]$$

$$R_{min} \geq \frac{V_{BB} - V_V}{I_V} = \frac{12 - 2}{4 \times 10^{-3}} \geq [2.5\text{k}\Omega]$$

Assume $C = 0.02\mu\text{F}$

$$R = \frac{1}{f C \ln \frac{1}{1-\eta}} = 1005.78 \text{ k}\Omega$$

$R > R_{\max}$.

∴ Let $C = 0.04 \mu F$.

$$R = \frac{1}{f C \ln \frac{1}{1-\eta}} = 502.89 \text{ k}\Omega$$


∴ $R_{\min} < R < R_{\max}$ or $2.5k < 502k < 788k$

Hence R & C is acceptable.

$$\begin{aligned} \text{Here } R_{\text{TOT}} &= R_{\min} + R = 502.89k + 2.5k \\ &= 505.3k\Omega < R_{\max} \end{aligned}$$

$$\textcircled{B} \quad R_2 = \frac{10^4}{\eta V_{BB}} = 1.32 \times 10^3 \Omega$$

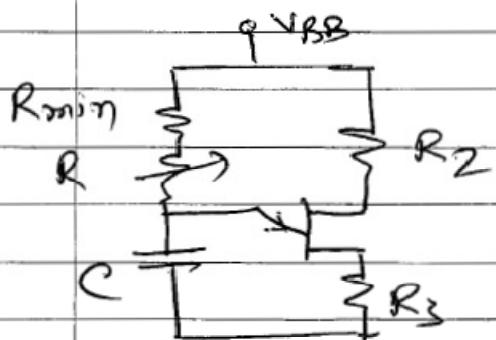Note: When emitter open drop across R_3 should not trigger SCR.



$$\therefore \frac{V_{BB} * R_3}{R_2 + R_3 + R_{BB}} < V_{trig}$$

$$\text{or } R_3 < \frac{V_{trig} (R_2 + R_{BB})}{(V_{BB} - V_{trig})}$$

$$R_3 < 103 \Omega$$

Minimum & Max firing time.

$$T_{\min} = R_{\min} C \ln \frac{1}{1-\eta}$$

$$T_{\min} = 0.0994 * 10^{-3} \text{ sec.}$$

Supply volt is 50 Hz or $T = 20 \text{ msec.}$

$$\therefore Lle \text{ in degrees/msec} = \frac{360}{20 * 10^{-3}}$$

$$\therefore Lle \text{ for } T_{\min} = 0.0994 * 10^{-3} * \frac{360}{20 * 10^{-3}}$$

$$\text{or } 0.994 * 18^\circ = \boxed{17.9^\circ}$$

As $Lle = 18^\circ / \text{msec.}$

$$T_{\max} = R_{\max} C \ln \frac{1}{1-\eta} = 19.98 \text{ msec}$$

$$\therefore \text{Max } Lle = 19.98 * 18^\circ = \boxed{359.7^\circ}$$

Ques (10) A UJT is connected across a 20V DC supply. The valley volt and peak volt are 1V and 15V respectively. The period of UJT relaxation oscillator is 20msec. Find values of charging cap if

Charging resistor is 100 k Ω . Assume $V_f = 0.8V$

~~8/5/92~~

VTU E&E 95 : 8mICL

$$V_p = \eta V_{BB} + V_v \text{ @ } \therefore \eta = \frac{V_p - V_v}{V_{BB}}$$

$$\eta = \frac{15 - 0.8}{20} = [0.71]$$

$$C = \frac{1}{TR \ln \frac{1}{1-\eta}} = [0.162 \mu F]$$

E&C May 98 8mICL VTU.

Prob (11) A UJT is used to trigger the thyristor whose min gate triggering voltage is 6.2V $\eta = 0.66$ $I_p = 0.5 \text{ mA}$ $I_V = 3 \text{ mA}$

$$R_{B1} + R_{B2} = 5 \text{ k}\Omega \quad I_{\text{Leakage}} = 3.2 \text{ mA}$$

$$V_p = 14 \text{ V} \quad V_v = 1 \text{ V} \quad \text{osc}^n f_{\text{req}} = 2 \text{ kHz}$$

$C = 0.04 \mu F$ Design the Ckt.

$$\text{Ans: } T = \frac{1}{RC \ln \frac{1}{1-\eta}} = [11.6 \text{ k}\Omega]$$

$$R_{\text{min}} \leq \frac{V_{BB} - V_p}{I_p} = 12 \text{ k}\Omega$$

$$R_{\text{min}} \geq \frac{V_{BB} - V_v}{I_v} = 6.33 \text{ k}\Omega$$

$$R_2 = \frac{0.7(R_{B1} + R_{E2})}{\eta V_{BB}} = [265\Omega]$$

$$V_{BB} = I_{leakage}(R_1 + R_2 + R_{B1} + R_{E2})$$

$$R_1 = \frac{V_{BB}}{I_{leakage}} - R_2 - R_{B1} - R_{E2}$$

$$[R_1 = 985\Omega]$$

Prob 12: Ang 95 smkd

Design the UJT ckt for SCR with

$$V_{BB} = 20V \quad \eta = 0.6, \quad I_p = 10mA, \quad V_T = 2V$$

$I_V = 10mA$ freq. = 100 Hz triggering Pulse width = $5\mu\text{sec}$

$$\text{Assume } C = 1\text{MF}, \quad V_T = 0.7V$$

$$R = \frac{1}{TC \ln \frac{1}{1-\eta}} = [10.911C\Omega]$$

$$R_{max} \leq \frac{V_{BB} - V_P}{I_P} = \frac{20 - 12.7}{10 \times 10^{-6}} = [0.73M\Omega]$$

$$V_P = \eta V_{BB} + V_T = 0.6 \times 20 + 0.7 = 12.7V$$

$$R_{min} > \frac{V_{BB} - V_V}{I_V} = \frac{20 - 2}{10 \times 10^{-3}} = \boxed{1.8 \text{ k}\Omega}$$

$$R_2 = \frac{10^4}{\eta V_{BB}} = \boxed{833.3 \Omega}$$

$$R_1 C \geq t_g \text{ or } R_1 \geq \frac{50 \times 10^{-6}}{1 \times 10^{-6}} = \boxed{50 \Omega}$$

$$\text{or } 5R_1 C \geq t_g \text{ or } \boxed{R_1 \geq 10 \Omega}$$